

FPGA Workshop

Introduction to Sequential Circuits


HacDC
Nov 2009.

Why Sequential?

- It helps when the regulator is in town
- Time can be used to regulate operations
 - I will be ready by tomorrow/one hour/(1/1Mhz)
- So far, we have implemented circuits that are asynchronous (meaning do not use a clock to regulate when the output becomes ready)
- This may be useful when you just have one function to implement, but is problematic if you need to implement functions in series.


Introducing the Clock

 - **Combinatorial vs Sequential logic**
- A defining feature of Sequential logic is the presence of a clock and a **memory** element
- Not only does the output depend on where we are in (clock) time, but also what were the previous outputs (memory)
- Will be used to create Finite State Machines
 - “Where am I? What has changed? Where should I go?”




Latch vs Flip Flop

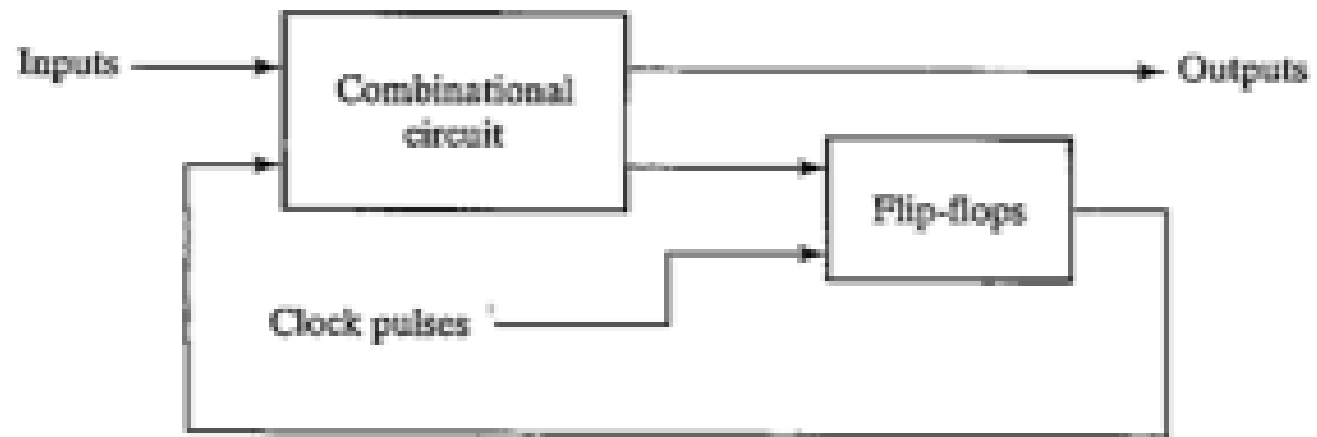- Often (historically) has been used interchangeably
 - In this class, we will define a distinction between the two, for logical reasons
 - All Latches/Flip Flops are defined by a function table
- **Latch** is a non-clocked memory
- **Flip Flop** is a Latch with a clock input




(a) Block diagram

 

(b) Timing diagram of clock pulses

Latches – SR Latch

- Set or Reset?
- Bistate vibrator!!

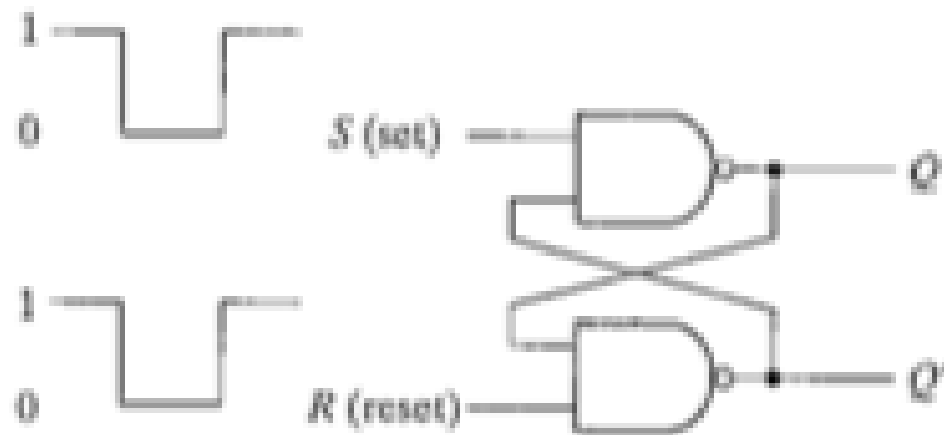

(a) Logic diagram


S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

(after $S = 1, R = 0$)
(after $S = 0, R = 1$)

(b) Function table

Latches – SR Latch

- Implemented with NOR Gates

 


(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

 (b) Function table

Latches - SR Latch

- Implemented with an additional **control input**




(a) Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

 (b) Function table

Latches – D Latch

- Simply follows the input
- An SR Latch with no ambiguous states




(a) Logic diagram

<i>C</i>	<i>D</i>	Next state of <i>Q</i>
0	X	No change
1	0	$Q = 0$; Reset state
1	1	$Q = 1$; Set state


(b) Function table

Latches - Symbols


- Circle means invert!

 

SR

 

SR

 

D

What to do with the Clock?

- Its useful to define a time period in which the output will be ready (e.g. high time, or low time)
- Even better, get locked to edge of the clock!



(a) Response to positive level




(b) Positive-edge response



 (c) Negative-edge response


Introducing the Flip Flop!

- Add a clock, and you have a Flip-Flop
- Output change in response to inputs **and** the clock!
- One way to implement an edge triggered Flip Flop is using a Master/Slave Implementation




Flip Flops – D

 
- Positive Edge Triggered Flip Flop using three SR Latches



Where to trigger?

 


(a) Positive-edge

 


(a) Negative-edge

Flip Flops - T

- Boring! but sometimes useful

 

(b) From *D* flip-flop

 

(c) Graphic symbol

Flip Flops - JK

- Badass flip-flop
- Allows you to set/reset or complement the previous input


Table 5-1
Flip-Flop Characteristic Tables

JK Flip-Flop			
<i>J</i>	<i>K</i>	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement


D Flip-Flop		
<i>D</i>	$Q(t + 1)$	
0	0	Reset
1	1	Set

T Flip-Flop		
<i>T</i>	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Flip Flops - JK

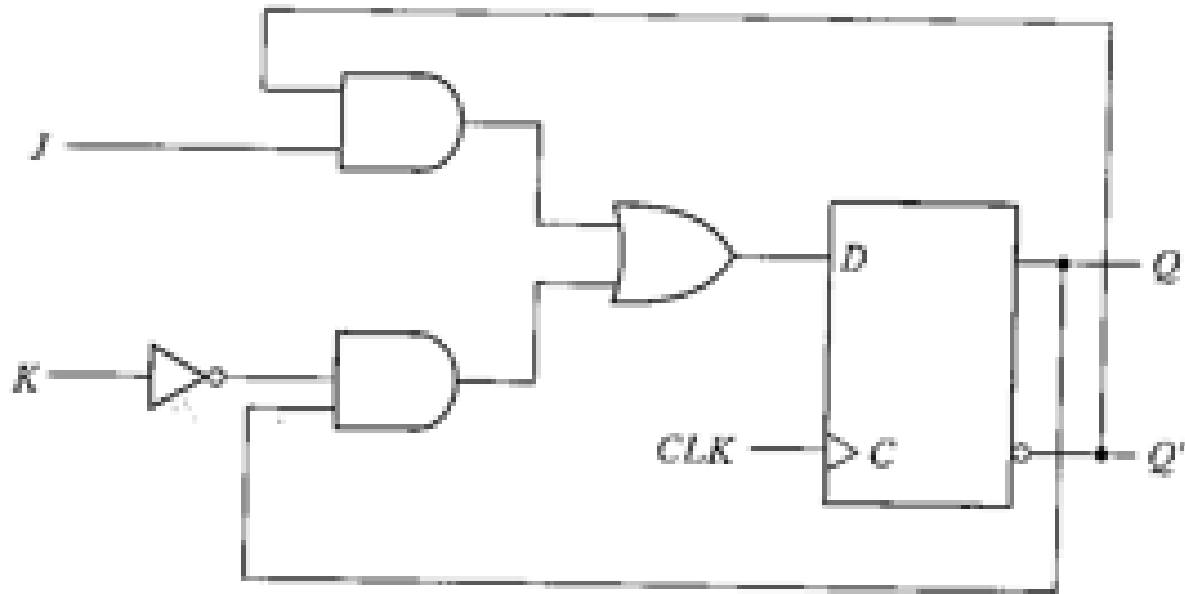


(a) Circuit diagram

 


(b) Graphic symbol

What if I want a flip flop with a hammer?

Asynchronous Reset

 

(a) Circuit diagram

 

(b) Graphic symbol

R	C	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(b) Function table

Fine.

Problems

-

-

-

-

- None.

-

-

-