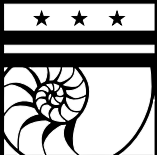


Intro to Electronics


Week 3



Thanks to EMSL for the idea:
<http://www.evilmadscientist.com/article.php/nightlight>


Make a night light

TODAY'S PROJECT


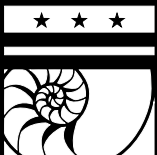


LED


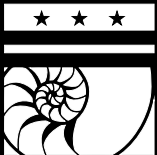
- Remember these?
- What does it take to light one?



Go ahead and do it

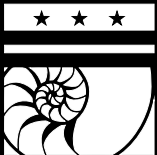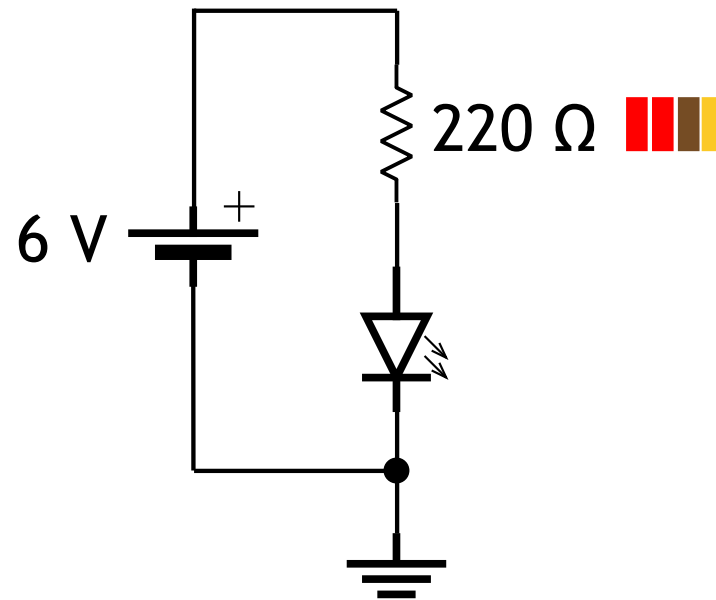


Go ahead and do it

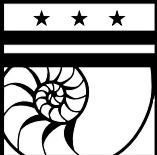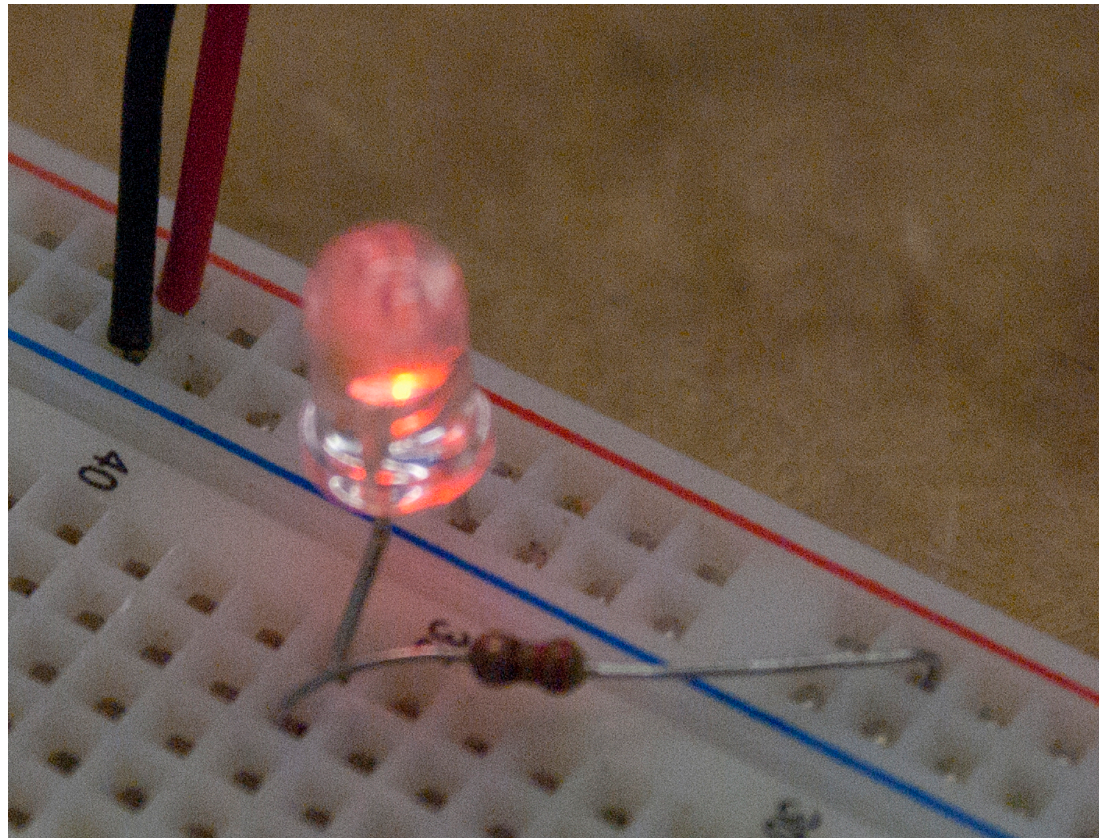


Transistor

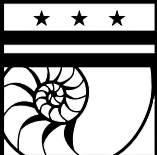- “The fundamental building block of modern electronic devices” (Wikipedia)




Why so important?

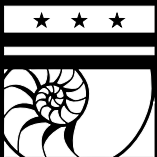- Amplification
 - Make a small input change cause a large output change
 - Useful for audio and radio




Why so important?

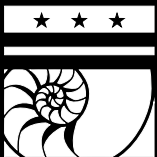- Switching
 - Control whether something else turns on or off
 - Useful for digital logic and control





Bipolar junction transistor

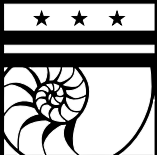- Common transistor type
 - Only one we'll use in this class
 - We'll just use it for switching





BJT

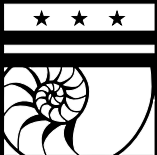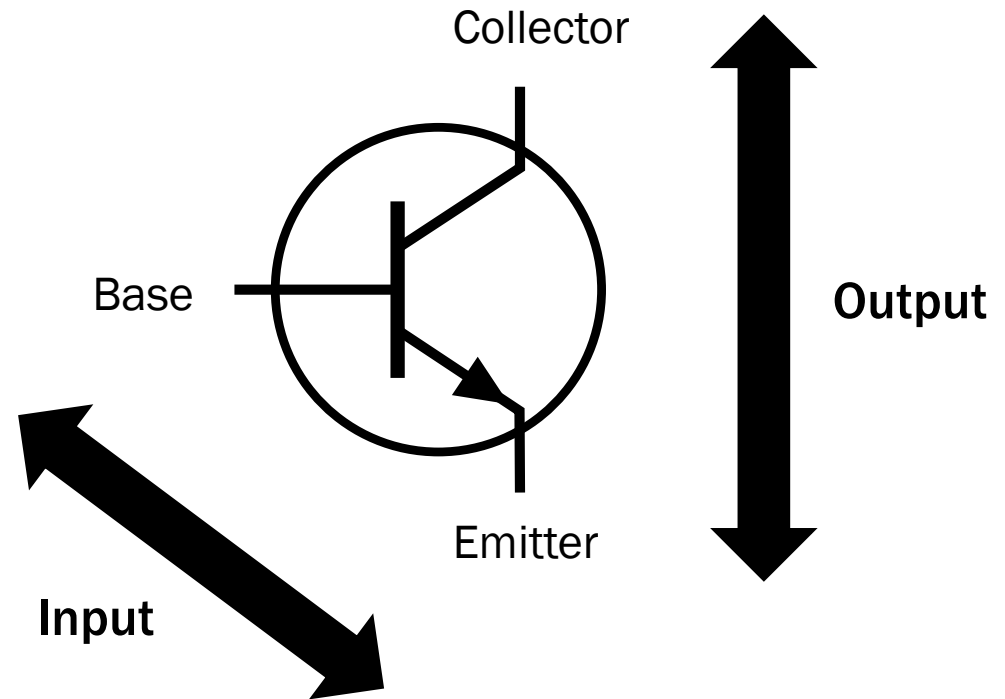- Three terminals
 - Base
 - Emitter
 - Collector





BJT

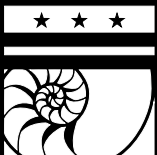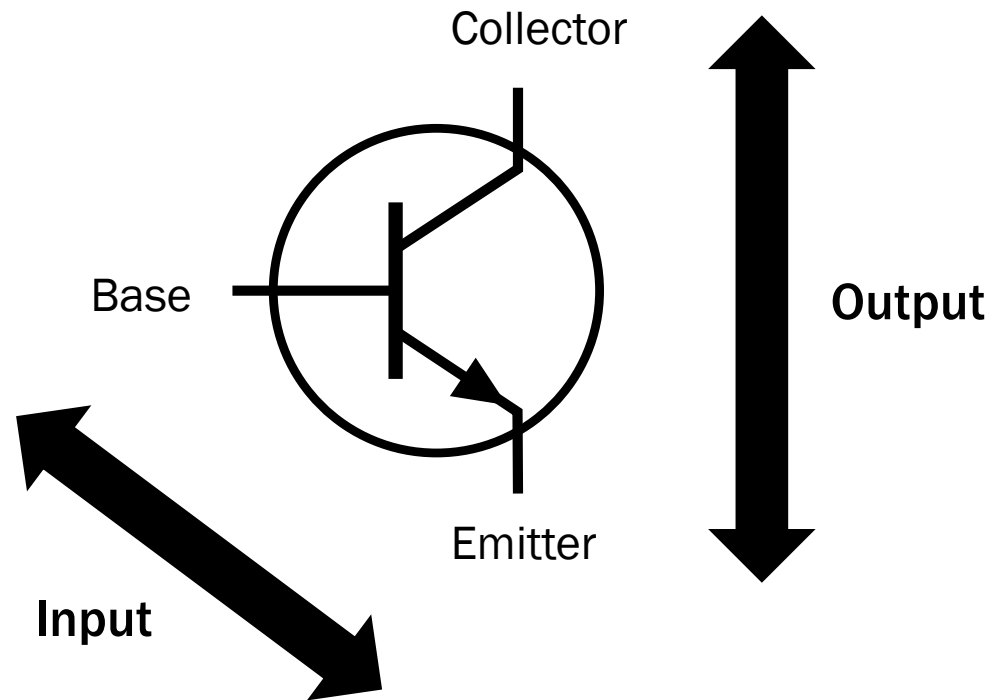- Current flows into base
- Transistor allows current to flow into collector
- Both currents come out the emitter
 - Hence the arrow pointing out




Let's add one

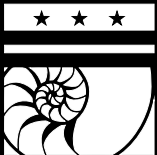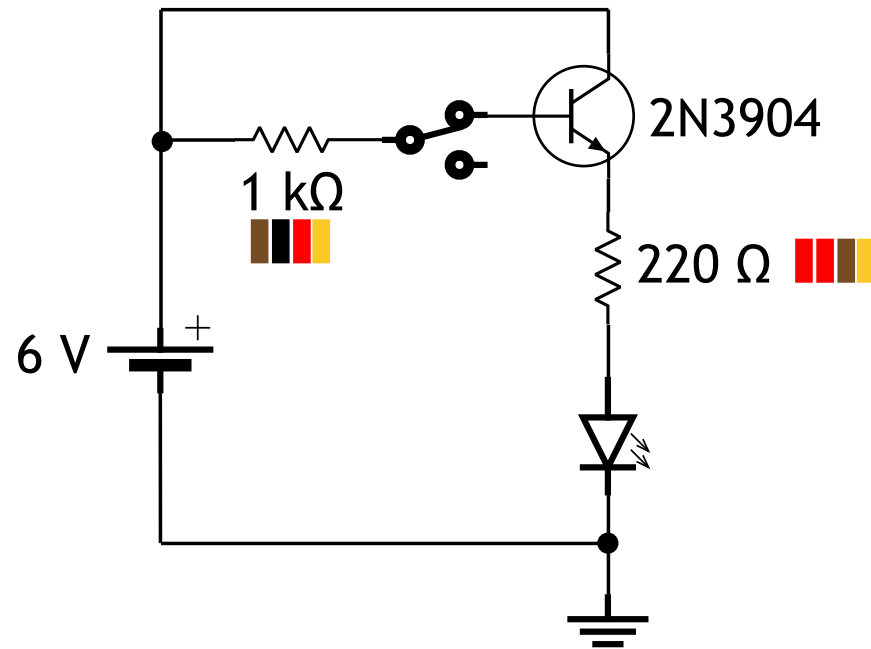



Sort of boring, right?

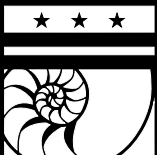- No real difference from before
 - Switch turns transistor on and off
 - Transistor turning on and off makes LED do the same
- Need another way to control the transistor





Phototransistor

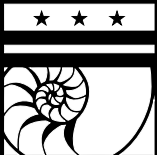
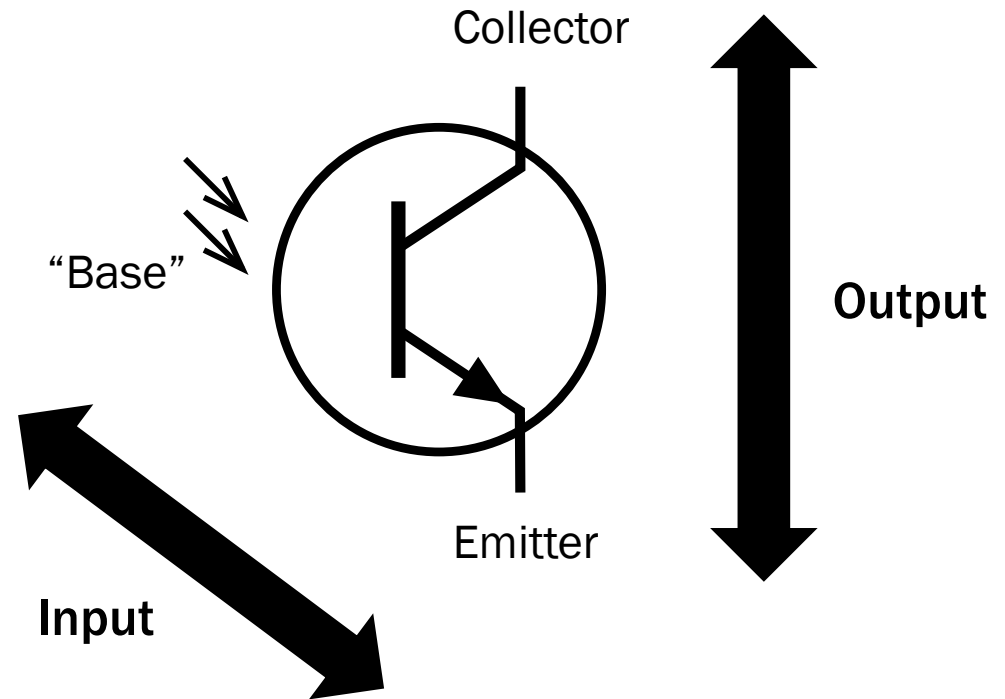
- Instead of supplying base current, shine a light on it!



Let's add one

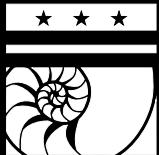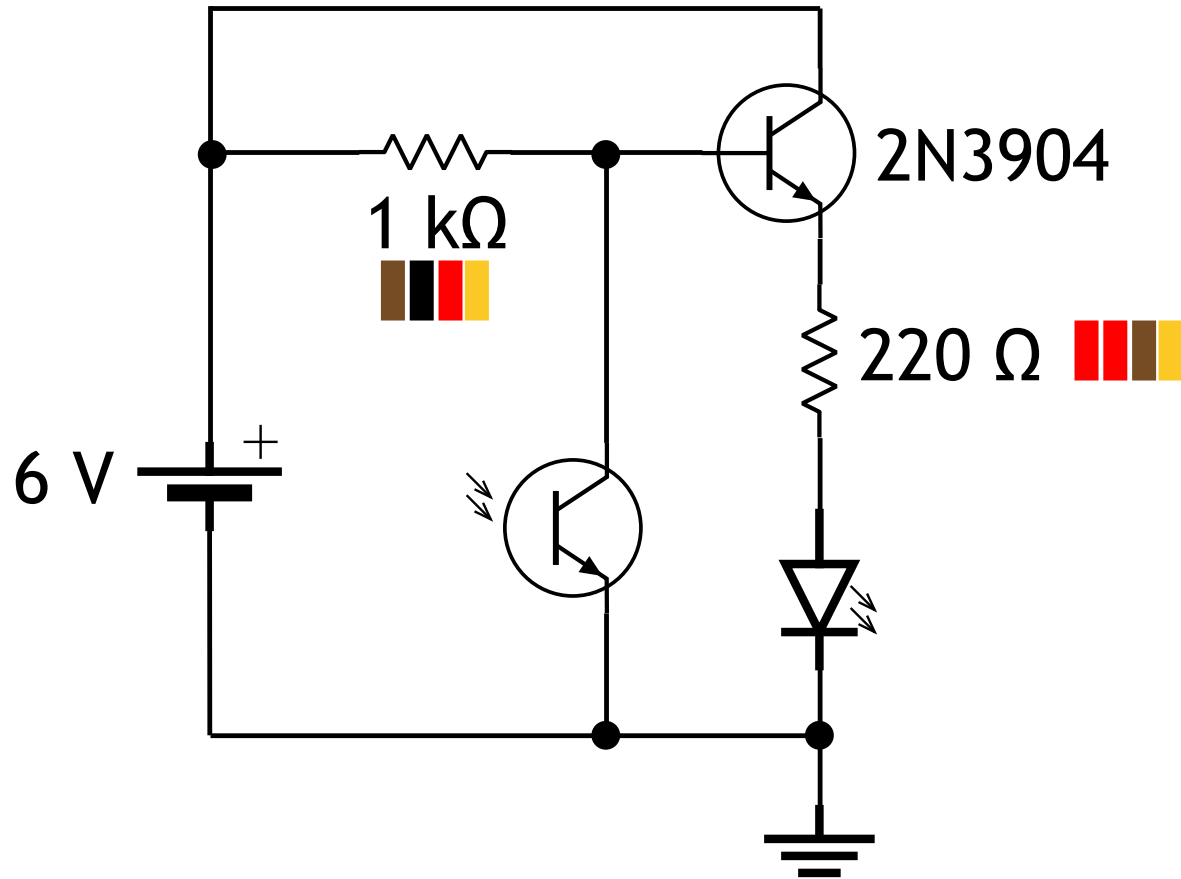


Let's add one

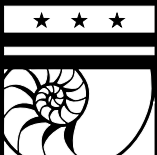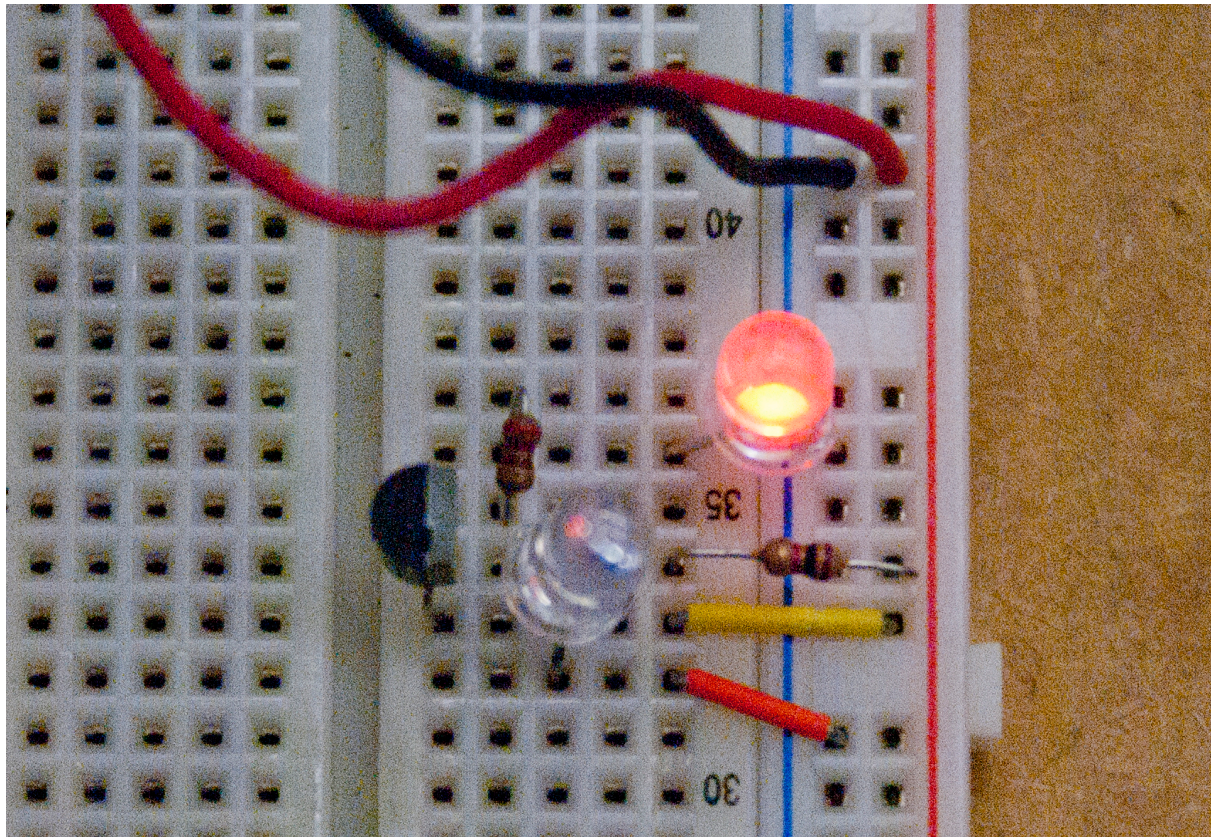


What happens?

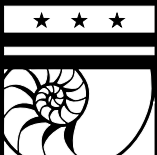- Light shines on the phototransistor
- Base current no longer goes to BJT
 - Goes straight to ground instead
- BJT turns off → LED turns off





Why isn't this working?

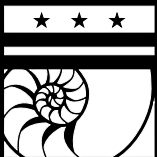- Phototransistors tend to be sensitive to just one kind of light
 - In this case: Infrared (most common case)
- Fluorescent lights don't put out much infrared
 - Try another light (or the sun!)




Why two transistors?

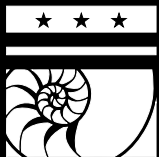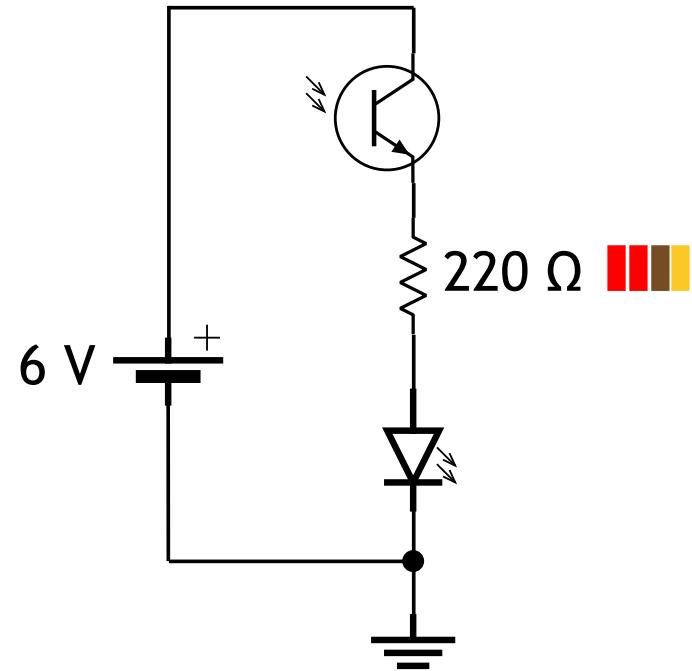- Without them, we'd have a day light, not a night light




A thought

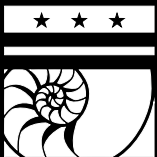- We just used one transistor to control another transistor!
 - Beginning of digital logic




Digital logic

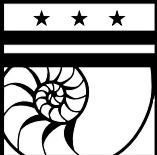- Combine switches to do exciting things!
- Basic building blocks: Logic gates
 - Can be made entirely of transistors




Logic gates

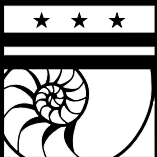- Take one or more inputs
- Follow some sort of rules
- Produce an output



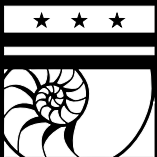
Examples

- AND gate: Two inputs
 - If they're both on, the output's on
 - Otherwise, the output's off
- OR gate: Two inputs
 - If either one is on, the output's on
 - Otherwise, the output's off



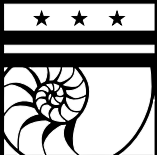
Examples

- NOT gate: One input
 - If it's on, the output's off
 - Otherwise, the output's on





Back to the night light

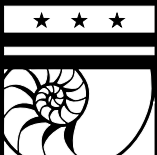
- You just made a NOT gate!
 - If the input's on...
 - There's ambient light
 - ...the output's off!
 - The LED stays unlit
 - If the input's off...
 - There's no ambient light
 - ...the output's on!
 - The LED lights up



Compare

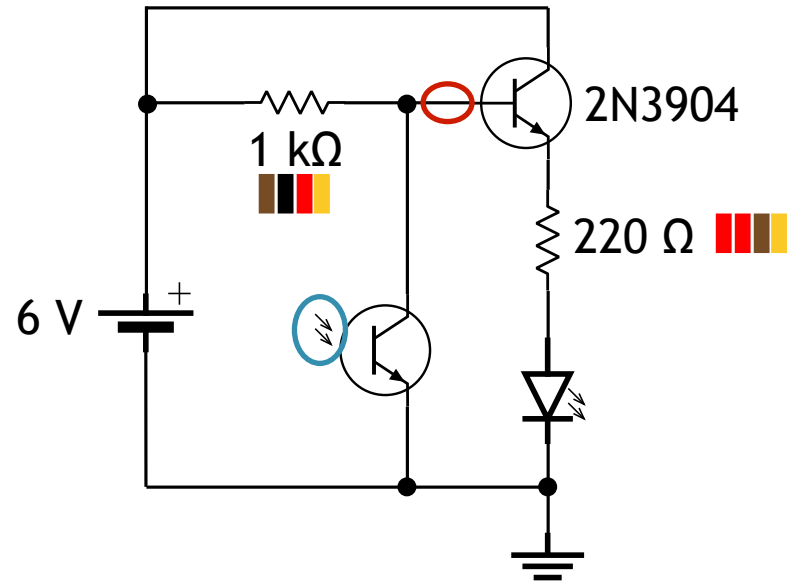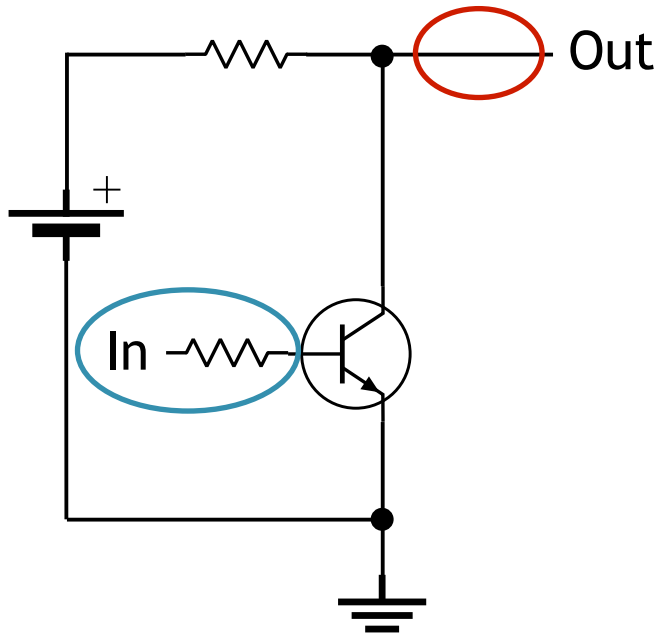

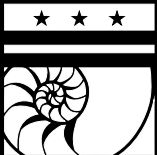
<http://www.kpsec.freeuk.com/trancirc.htm#inverter>



Remember this

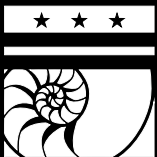- We'll do more with logic in a couple of weeks
 - We'll use premade gates and such, though



That's it for tonight

- Next week
 - Oscillators
 - Timers

