

L12: Reconfigurable Logic Architectures



Acknowledgements:

Materials in this lecture are courtesy of the following sources and are used with permission.

Frank Honore

Prof. Randy Katz (Unified Microelectronics Corporation Distinguished Professor in Electrical Engineering and Computer Science at the University of California, Berkeley) and Prof. Gaetano Borriello (University of Washington Department of Computer Science & Engineering) From Chapter 2 of R. Katz, G. Borriello. Contemporary Logic Design. 2nd ed. Prentice-Hall/Pearson Education, 2005.

- Discrete devices: relays, transistors (1940s-50s)
- Discrete logic gates (1950s-60s)
- Integrated circuits (1960s-70s)
 - e.g. TTL packages: Data Book for 100's of different parts
- Gate Arrays (IBM 1970s)
 - Transistors are pre-placed on the chip & Place and Route software puts the chip together automatically – only program the interconnect (mask programming)
- **Software Based Schemes (1970's- present)**
 - Run instructions on a general purpose core
- **Programmable Logic (1980's to present)**
 - A chip that be reprogrammed after it has been fabricated
 - Examples: **PALs**, EPROM, EEPROM, PLDs, **FPGAs**
 - Excellent support for mapping from Verilog
- **ASIC Design (1980's to present)**
 - Turn Verilog directly into layout using a library of standard cells
 - Effective for high-volume and efficient use of silicon area

- **Logic blocks**


- To implement combinational and sequential logic

- **Interconnect**

- Wires to connect inputs and outputs to logic blocks


- **I/O blocks**

 - Special logic blocks at periphery of device for external connections




- **Key questions:**

 - How to make logic blocks programmable? (after chip has been fabbed!)
- What should the logic granularity be?
- How to make the wires programmable? (after chip has been fabbed!)
- Specialized wiring structures for local vs. long distance routes?
- How many wires per logic block?



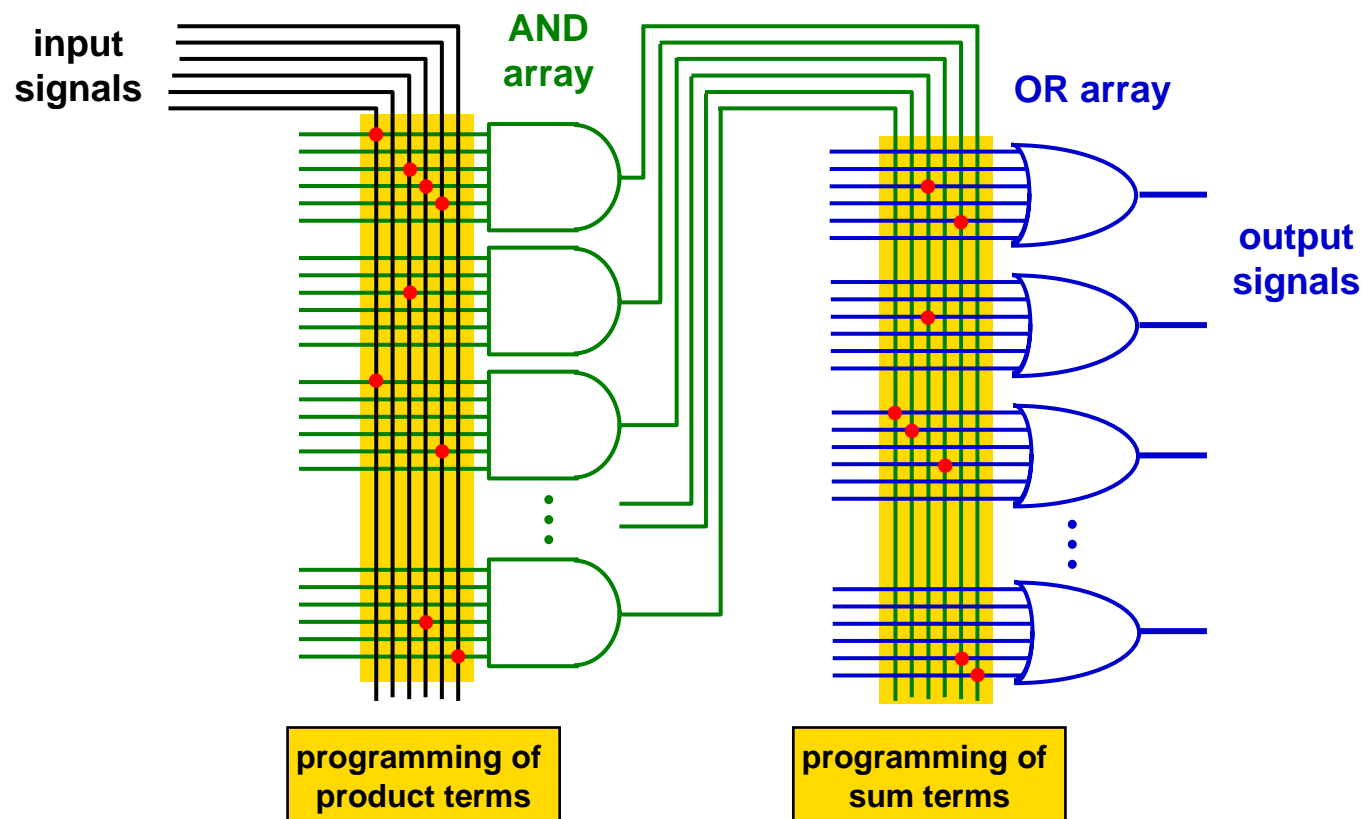
- Based on the fact that any combinational logic can be realized as a sum-of-products
- PALs feature an array of AND-OR gates with programmable interconnect




- Each input pin (and its complement) sent to the AND array
- OR gates for each output can take 8-16 product terms, depending on output pin
- “Macrocell” block provides additional output flexibility...

Image removed due to copyright restrictions.


Image courtesy of wikimedia

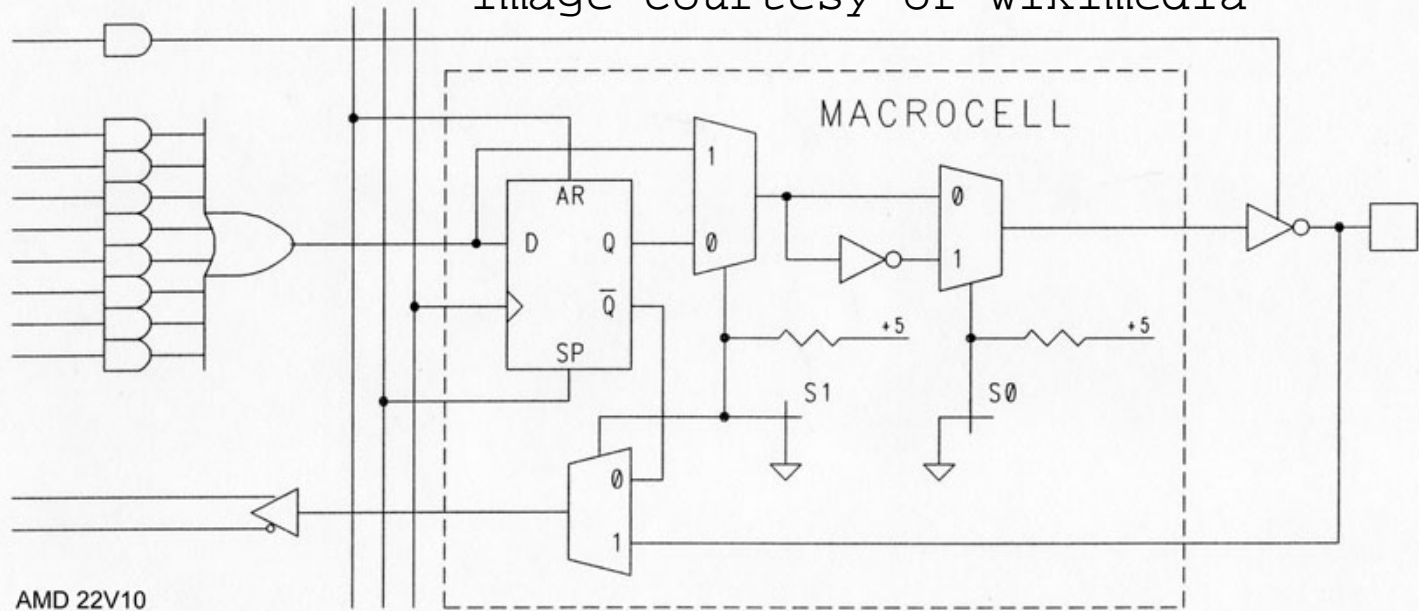

AMD 22V10

 

From Lattice Semiconductor

 

Images courtesy of Lattice Semiconductor Corporation. Used with permission.


S_1	S_0	Output Configuration
0	0	Registered/Active Low
0	1	Registered/Active High
1	0	Combinatorial/Active Low
1	1	Combinatorial/Active High

0 = Programmed EE bit


1 = Erased (charged) EE bit

- **Outputs may be registered or combinatorial, positive or inverted**

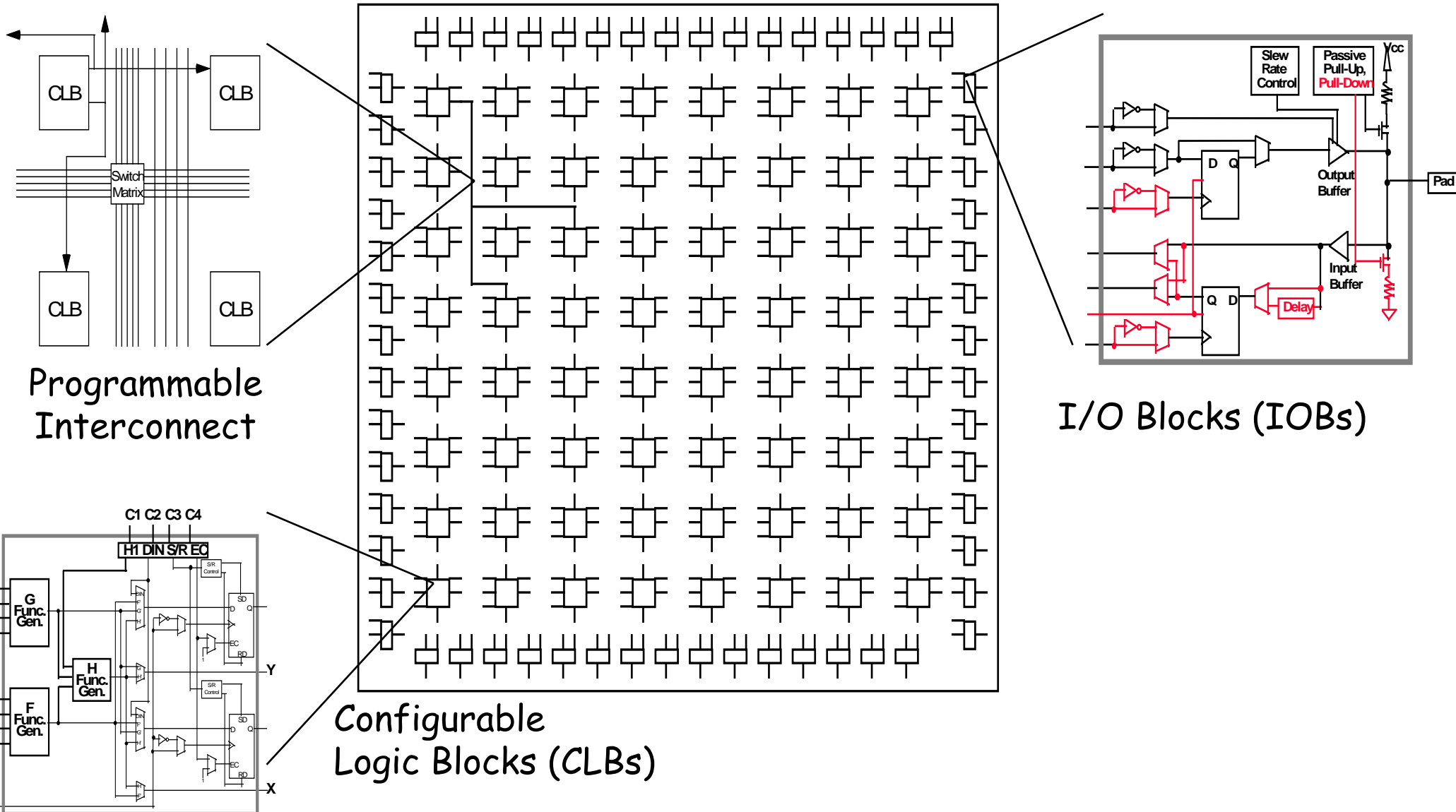RAM Based Field Programmable Logic - Xilinx



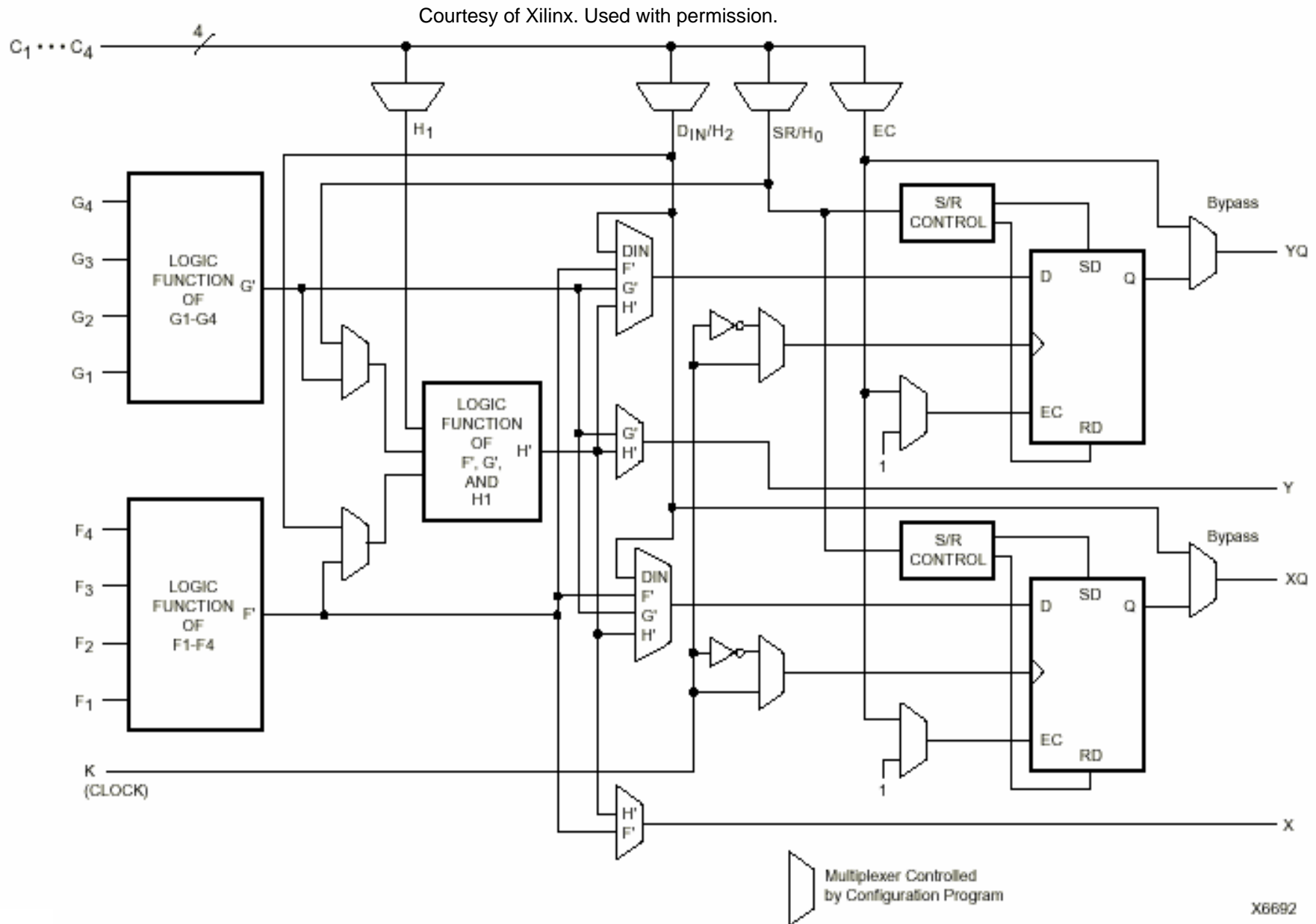
Courtesy of Xilinx. Used with permission.



Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)


Two 4-input Functions, Registered Output and a Two Input Function

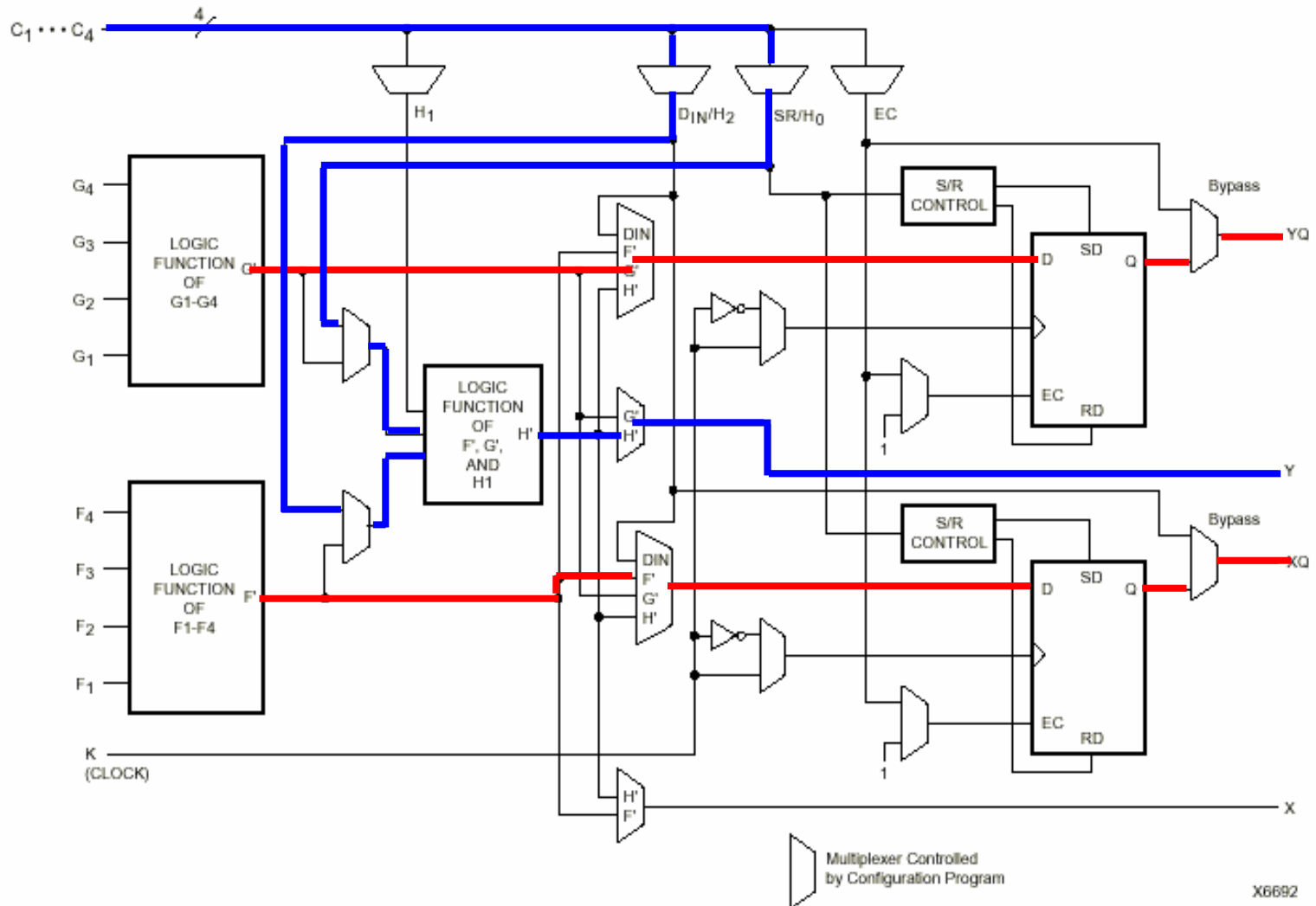Courtesy of Xilinx. Used with permission.




Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

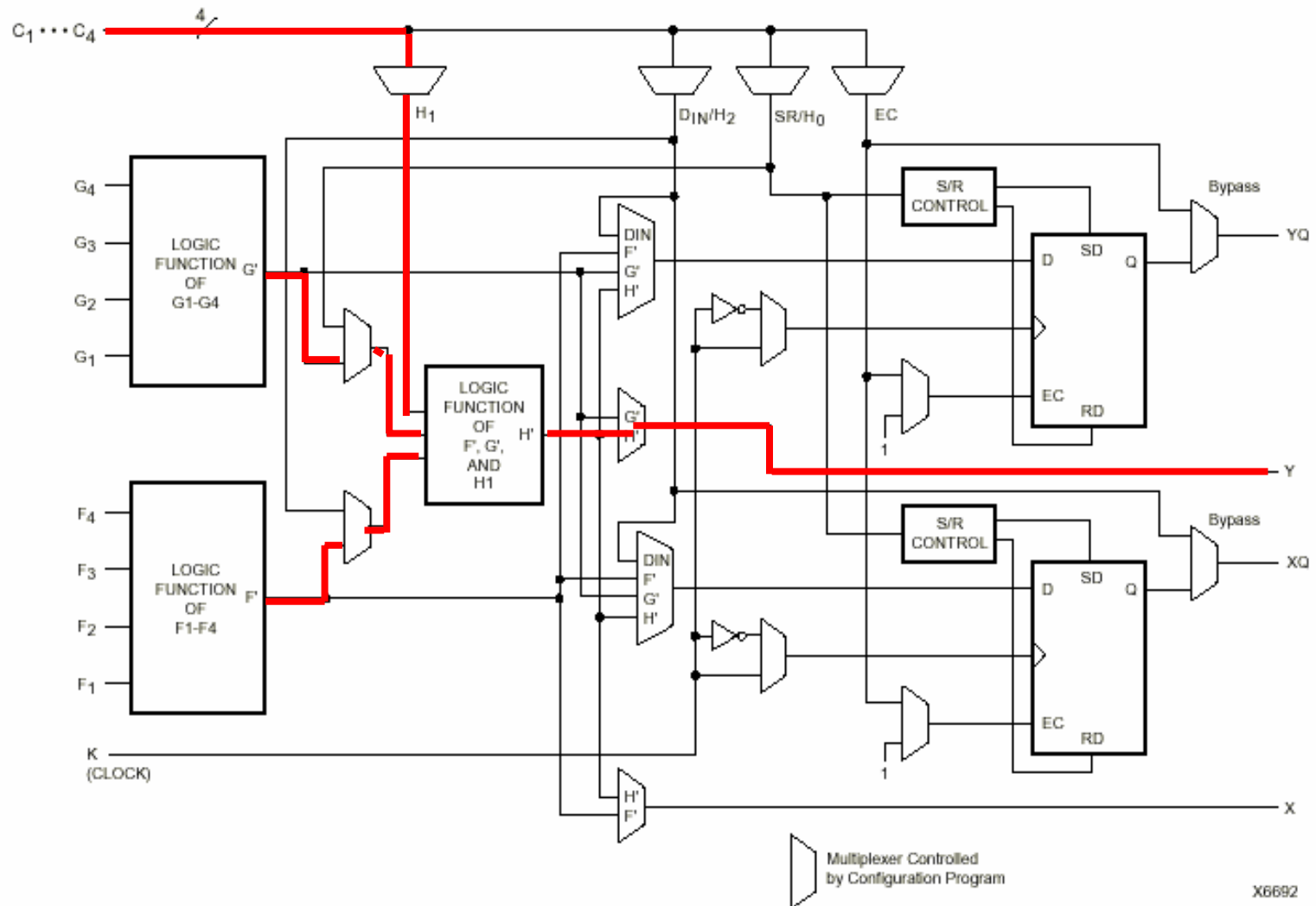Courtesy of Xilinx. Used with permission.



Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

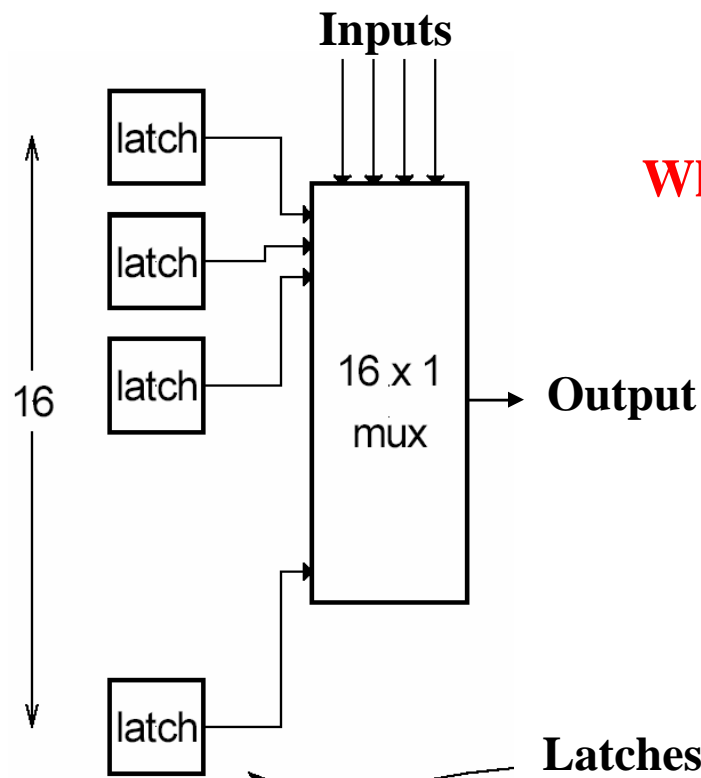
- N-LUT direct implementation of a truth table: any function of n-inputs.
- N-LUT requires 2^N storage elements (latches)
- N-inputs select one latch location (like a memory)



Why Latches and Not Registers?


Courtesy of Xilinx.
Used with permission.

4LUT example

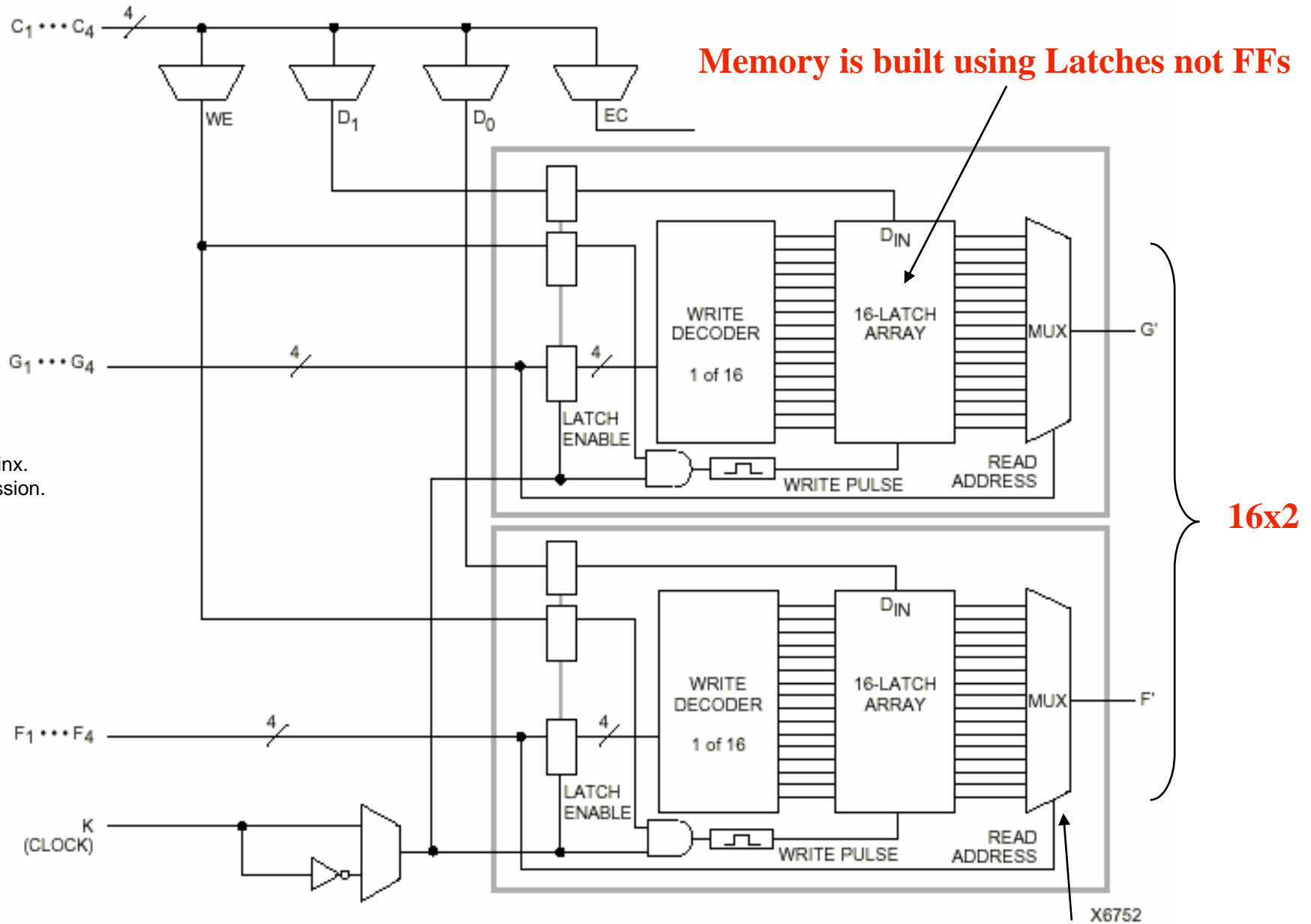



Courtesy of Xilinx.
Used with permission.

Read is same a LUT Function!

 


Single- and Double-Length Lines, with Programmable Switch Matrices (PSMs)

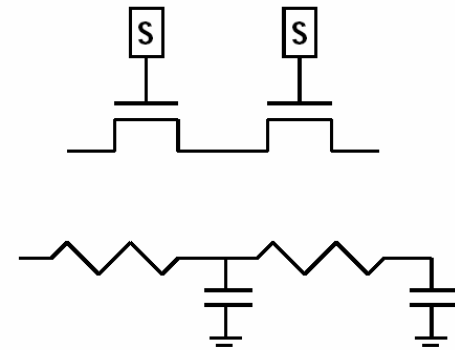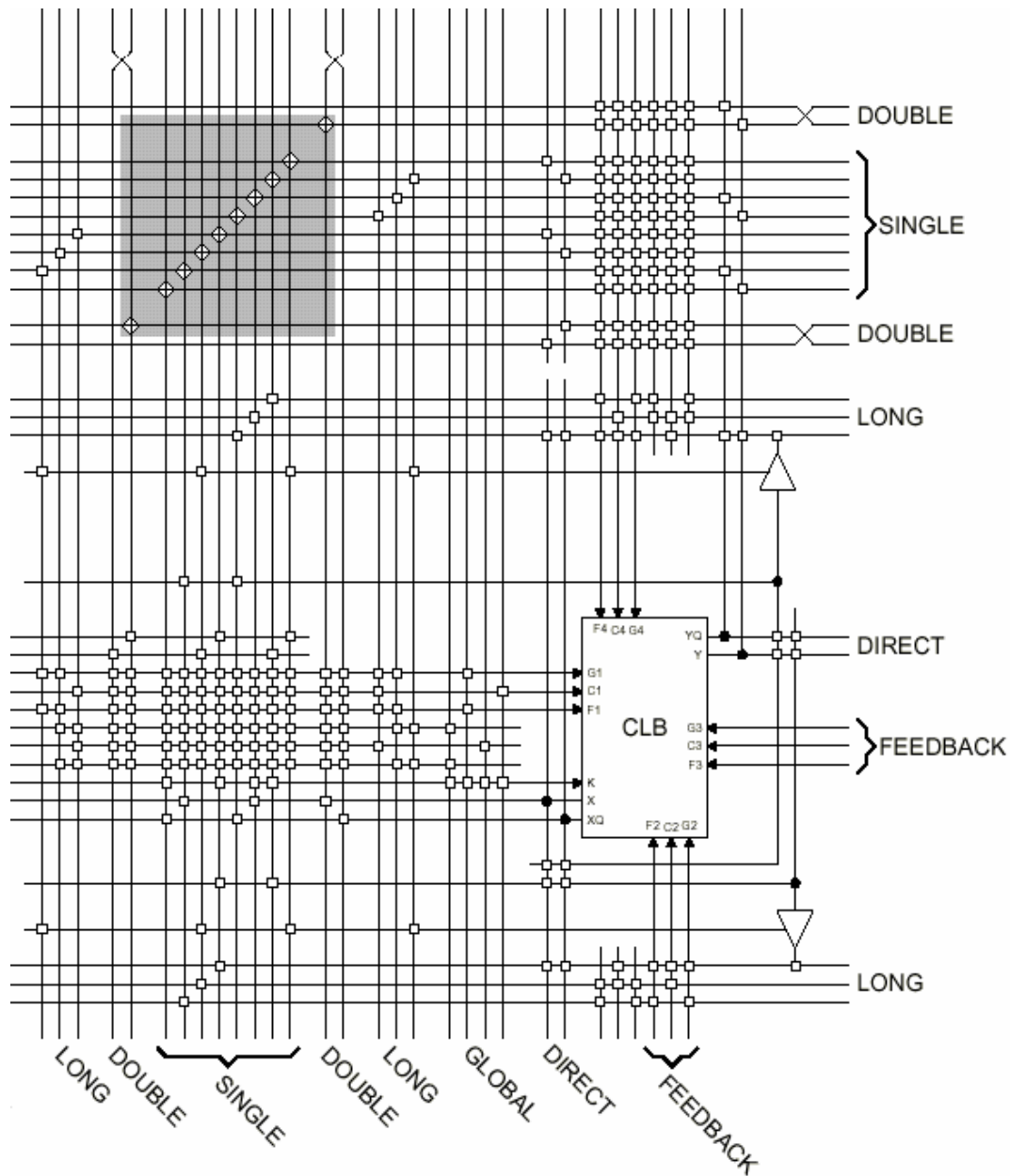Courtesy of Xilinx.
Used with permission.




Wires are not ideal!

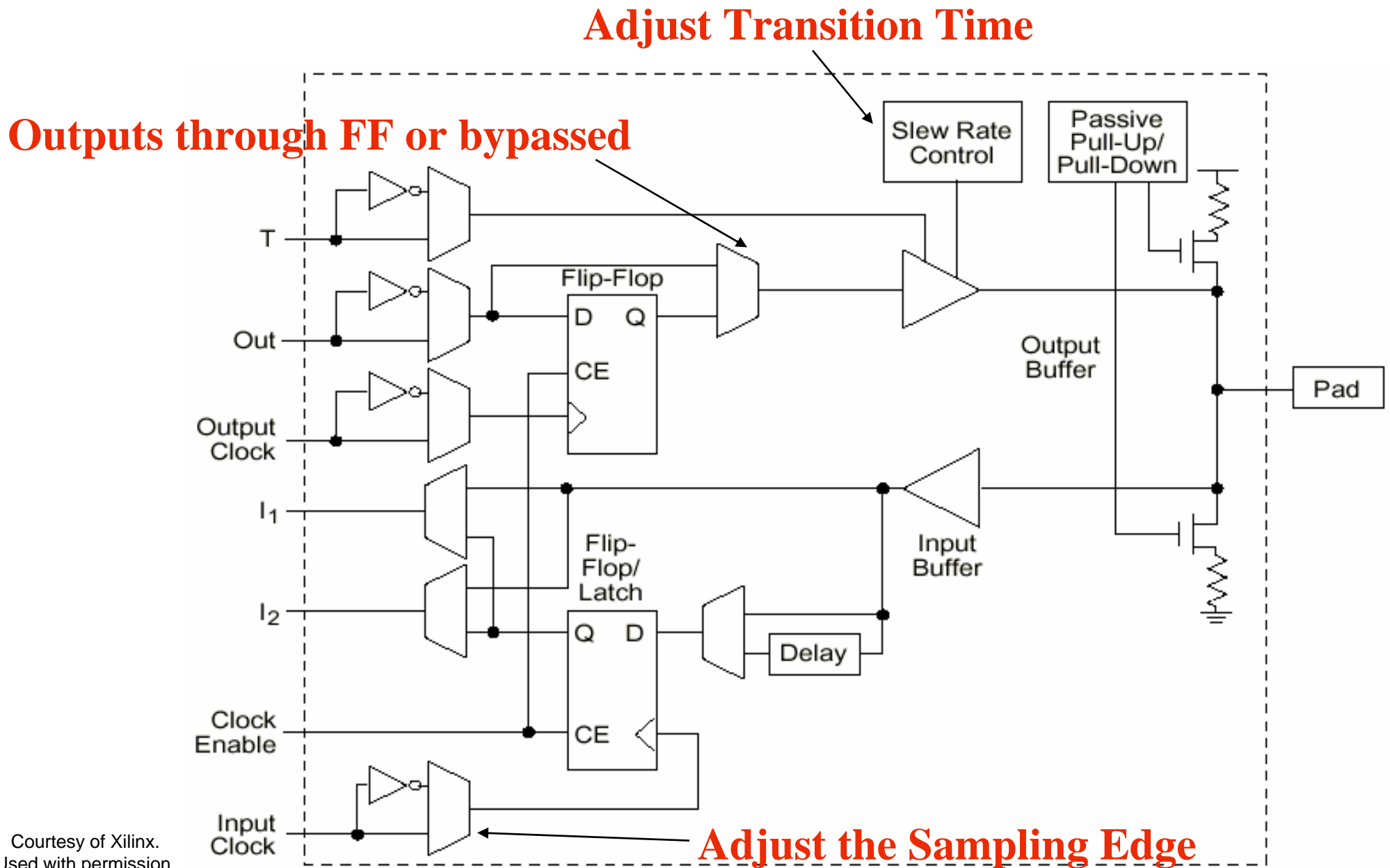
Courtesy of Xilinx.
Used with permission.



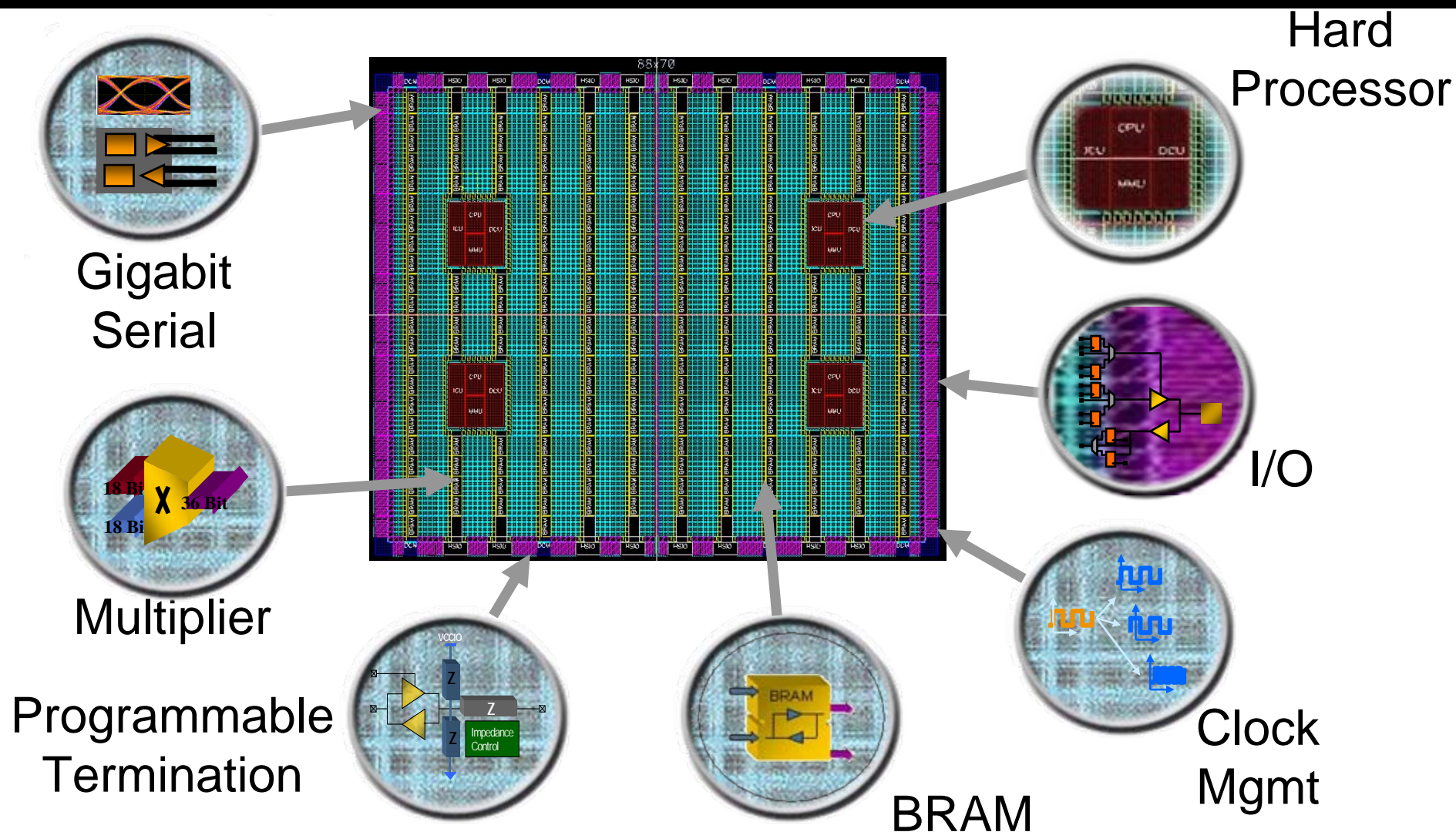Courtesy of Xilinx.
Used with permission.



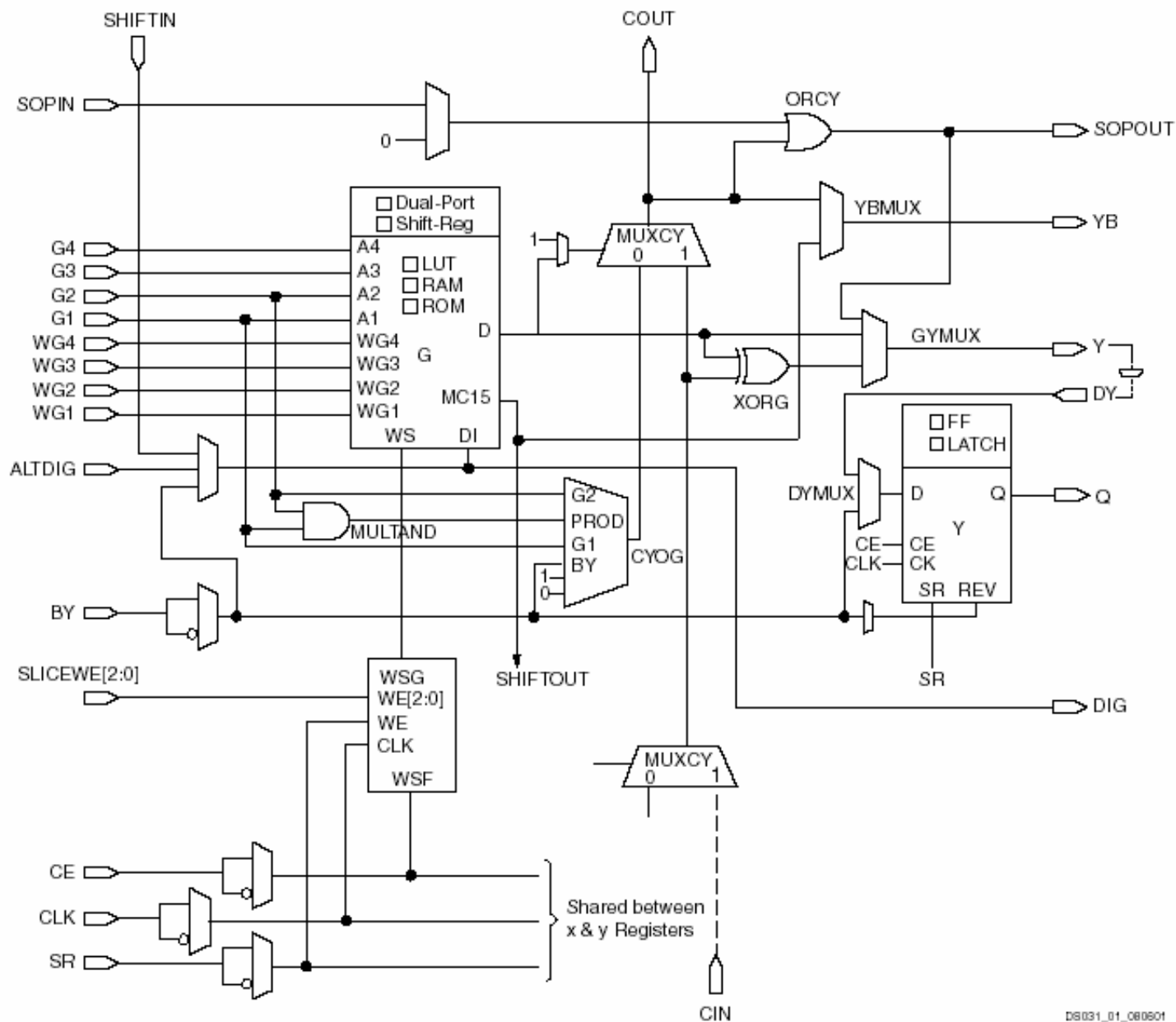
Courtesy of David B. Parlour, ISSCC 2004 Tutorial, "The Reality and Promise of Reconfigurable Computing in Digital Signal Processing." and Xilinx. Used with permission.



DS031_01_080501


Courtesy of Xilinx.
Used with permission.

Adder Implementation

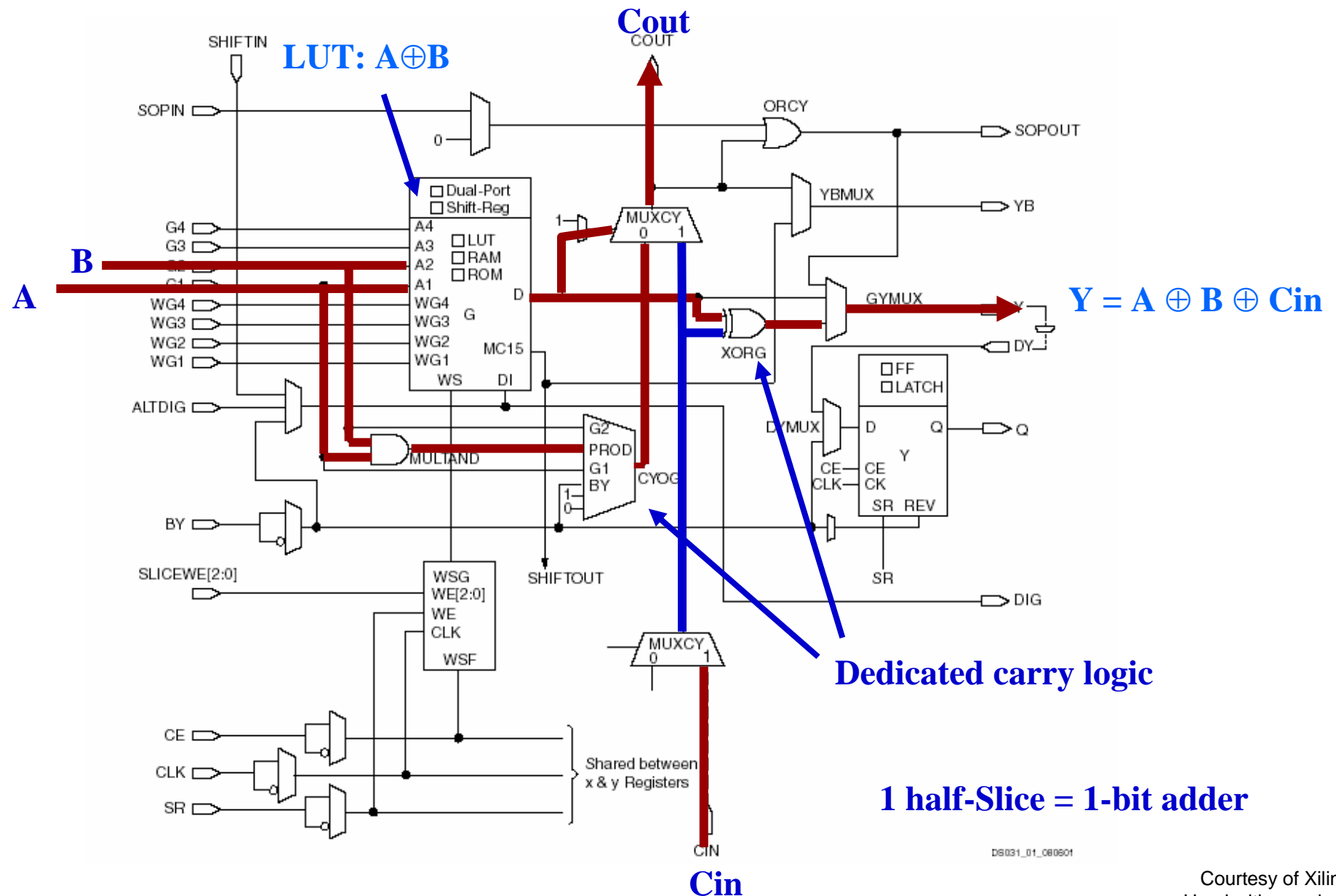



Courtesy of Xilinx. Used with permission.

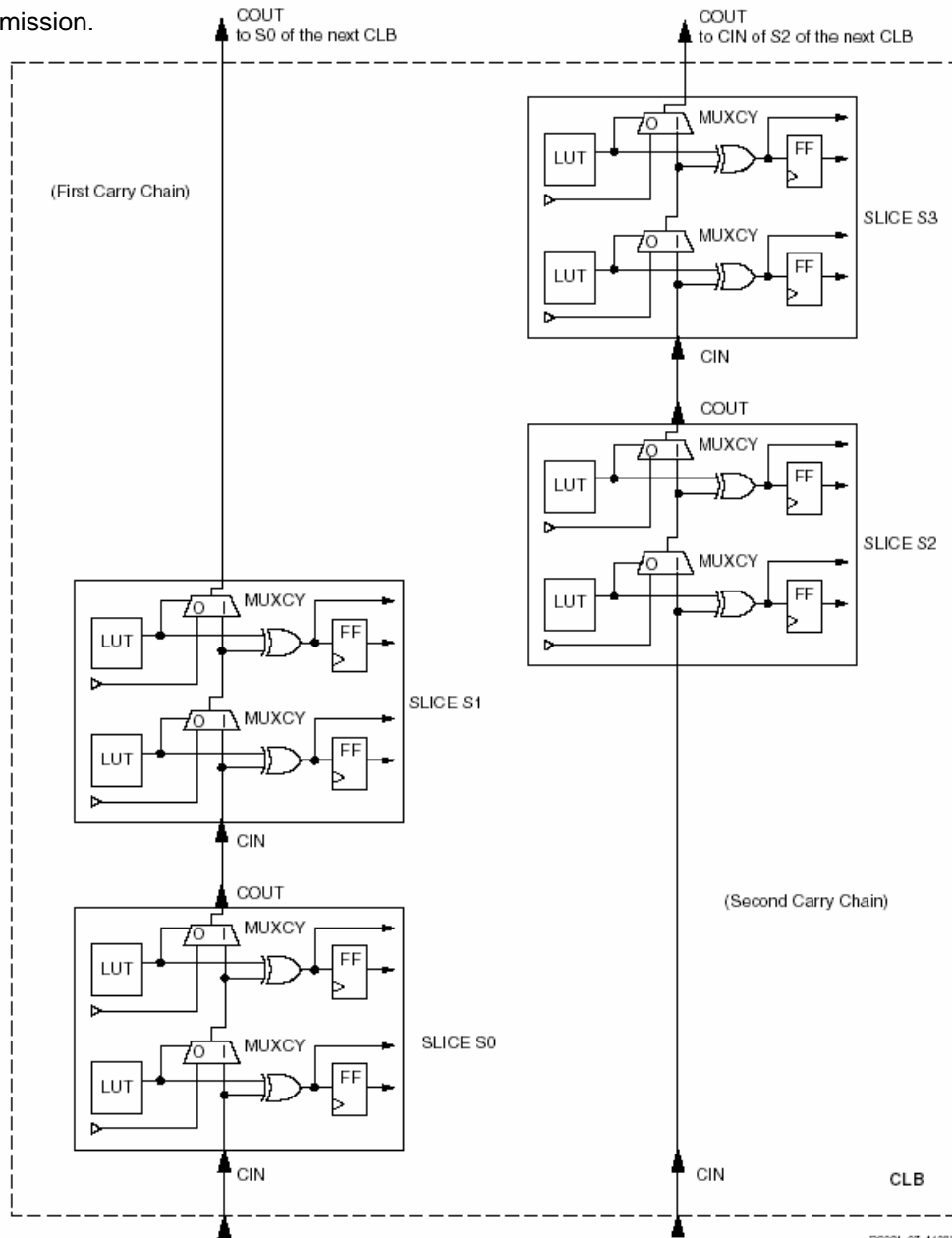Courtesy of Xilinx.
Used with permission.




1 CLB = 4 Slices = 2, 4-bit adders


64-bit Adder: 16 CLBs

  


CLBs must be in same column

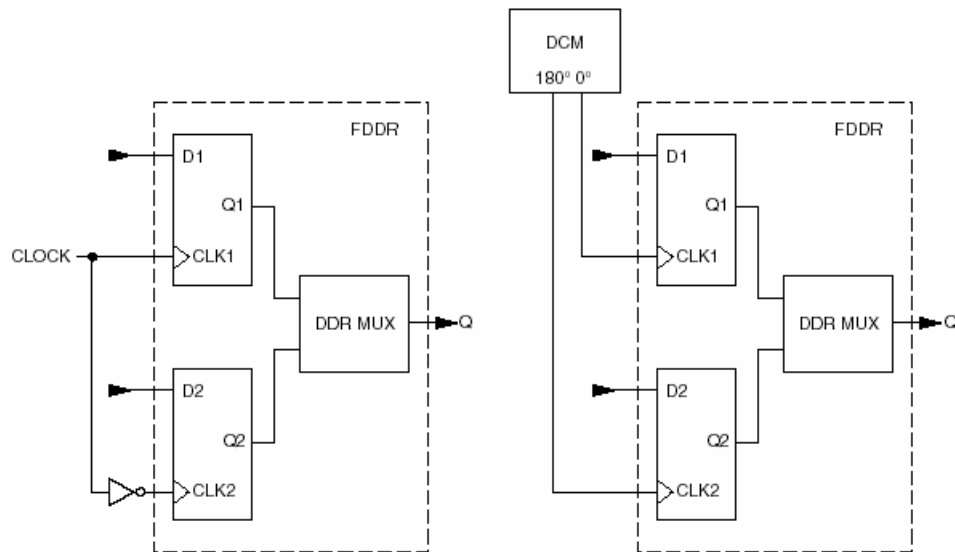


Double Data Rate registers

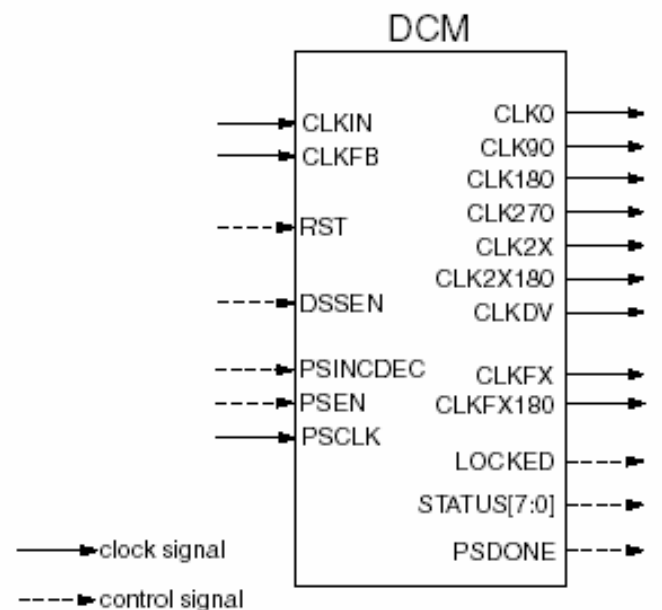

Digital Clock Manager


 


Embedded Multiplier

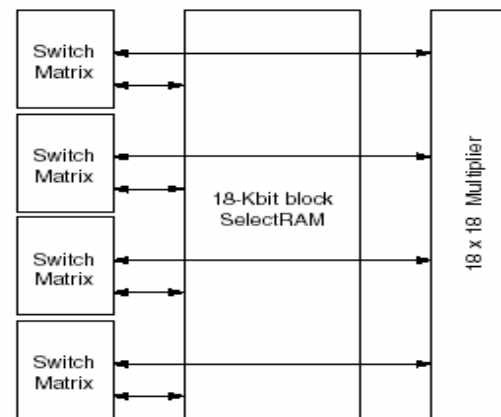


Block SelectRAM

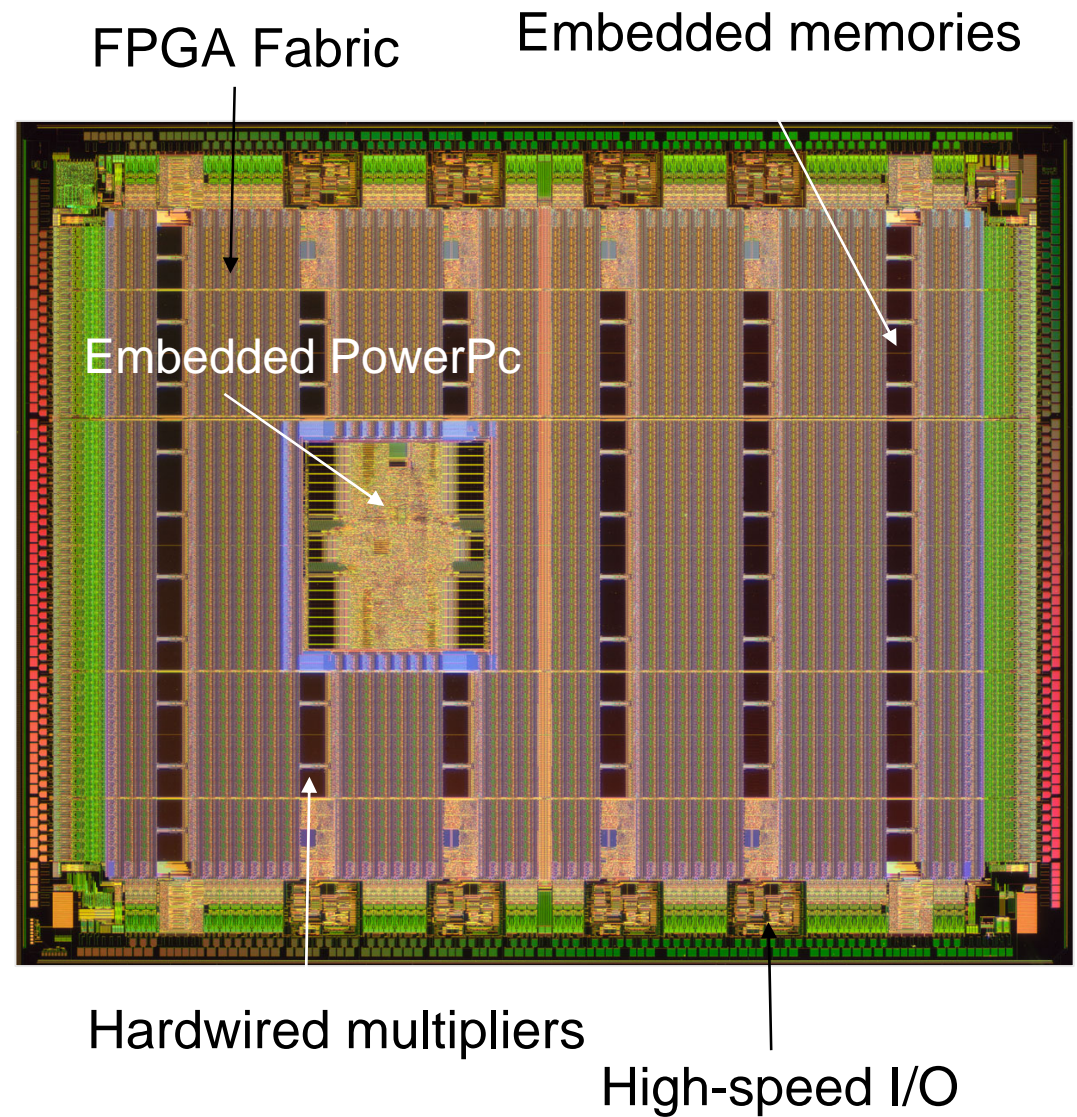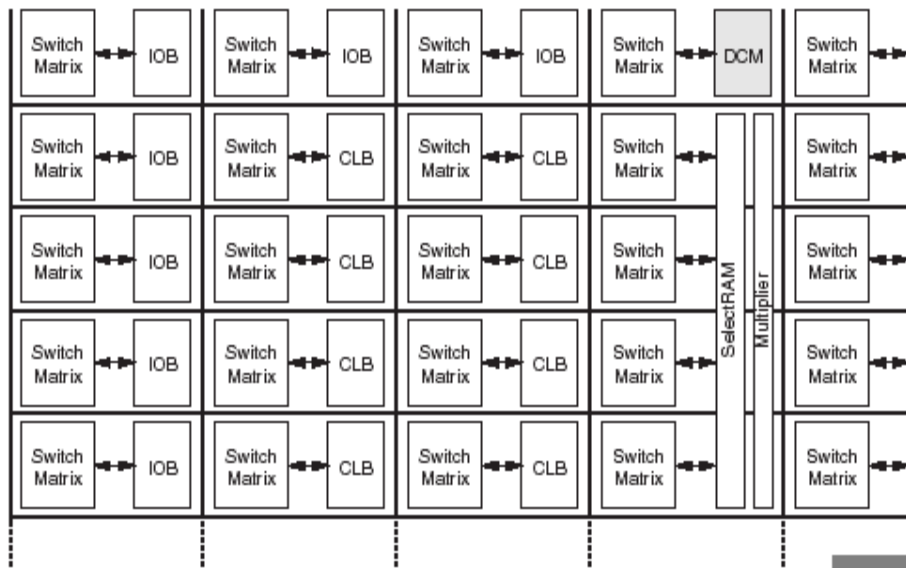Courtesy of Xilinx.
Used with permission.




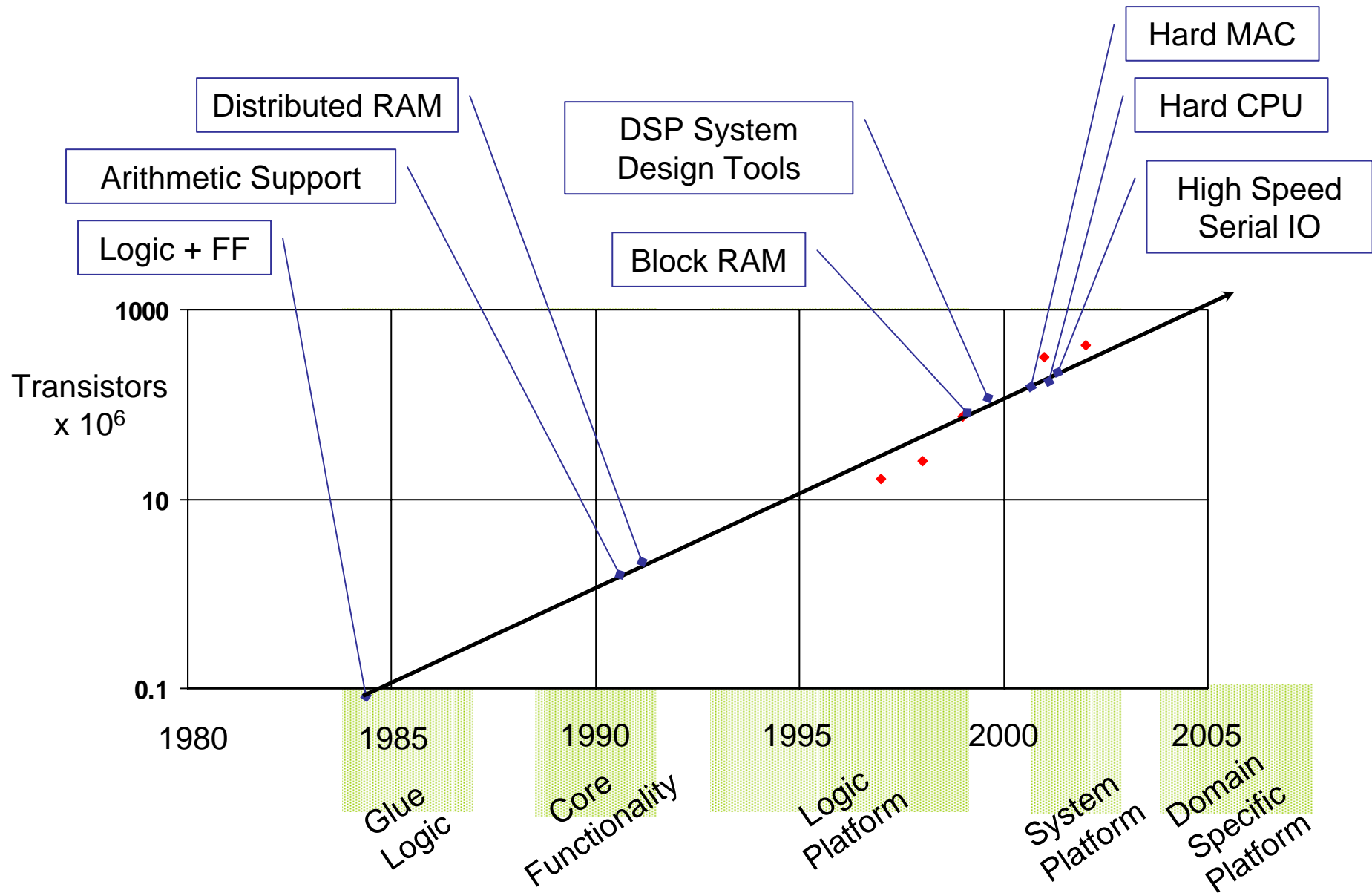Courtesy of Xilinx. Used with permission.



Courtesy of Xilinx. Used with permission.

 - **Technology Mapping: Schematic/HDL to Physical Logic units**
- **Compile functions into basic LUT-based groups (function of target architecture)**




```


always @(posedge Clock or negedge Reset)
begin
  if (! Reset)
    q <= 0;
  else
    q <= (a & b & c) | (b & d);
end

```

 
- **Placement** – assign logic location on a particular device



 - **Routing** – iterative process to connect CLB inputs/outputs and IOBs. Optimizes critical path delay – can take hours or days for large, dense designs



Iterate placement if timing not met

Satisfy timing? → Generate Bitstream to config device




Challenge! Cannot use full chip for reasonable speeds (wires are not ideal).

Typically no more than 50% utilization.

```

module adder64 (a, b, sum);
  input [63:0] a, b;
  output [63:0] sum;

  assign sum = a + b;
endmodule
  
```

  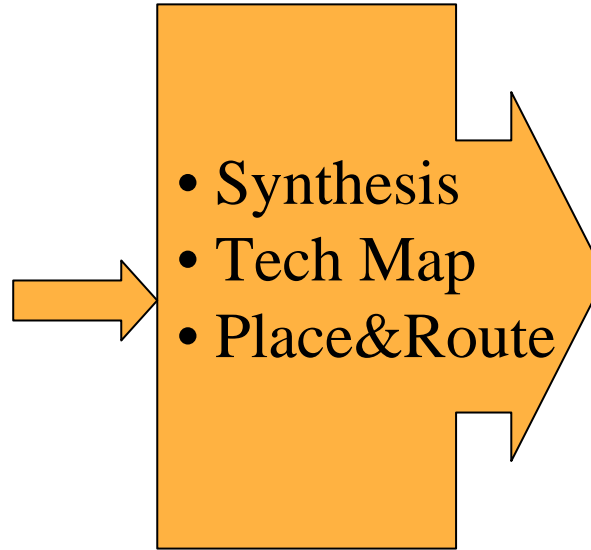

64-bit Adder Example

Virtex II – XC2V2000

Courtesy of Xilinx.
Used with permission.

- **Prototyping**
 - Ensemble of gate arrays used to emulate a circuit to be manufactured
 - Get more/better/faster debugging done than with simulation
- **Reconfigurable hardware**
 - One hardware block used to implement more than one function
- **Special-purpose computation engines**
 - Hardware dedicated to solving one problem (or class of problems)
 - Accelerators attached to general-purpose computers (e.g., in a cell phone!)

- **FPGA provide a flexible platform for implementing digital computing**
- **A rich set of macros and I/Os supported (multipliers, block RAMS, ROMS, high-speed I/O)**
- **A wide range of applications from prototyping (to validate a design before ASIC mapping) to high-performance spatial computing**
- **Interconnects are a major bottleneck (physical design and locality are important considerations)**

“College students will study concurrent programming instead of “C” as their first computing experience.”

-- David B. Parlour, ISSCC 2004 Tutorial