

Noisemaker Workshop

Attack of the Oscillator

April 22, 2009

Outline

Intro

Electronics Background

Oscillation

Attack of the Oscillator

Outline

Intro

Electronics Background

Oscillation

Workshop Overview

What's the plan?

- ▶ Today: Oscillators and a basic amplifier.
Driving speakers with interesting noise.
- ▶ Next week: Modulation.
Making stranger noises.
- ▶ Third week: Sequencers and rhythm generators.
Architecting the noise.
- ▶ Fourth week: Open lab. Special topics.
Digital oscillators? Voltage control? Serious modular synthesis?

Today: Building Simple Oscillators

What not to expect

- ▶ *Not* building what you probably think of as a synthesizer
- ▶ Not making something musical (yet).
(If by "musical" you mean sound that's based on melodies.)
- ▶ No keyboards

What to expect

- ▶ Many of the basic ideas of serious 1970's analog synthesis, in a stripped-down form
- ▶ Some electronics
- ▶ A lot of experimentation
- ▶ Bugs. Hardware bugs galore.

"There is no wrong way to do this..."

...is a complete lie

- ▶ This is not finger-painting, this is audio engineering.
- ▶ There are a couple of right ways and an infinity of wrong ways.
- ▶ The wrong ways are often interesting.
- ▶ Art is doing it the wrong way,
influenced by having practiced the right way.
- ▶ Hacking is just doing it, not worrying about right or wrong.
- ▶ We'll be starting out doing a number of things wrong.
- ▶ "There is no *wronger* way to do this?"

Quick Demo

Outline

Intro

Electronics Background

Oscillation

Electricity as Water

Two slide overview

- ▶ Electrical pressure (that can be used to get stuff done) is like water pressure.
Voltage = Pressure
- ▶ Electrical current (flowing electricity) is like flowing water.
Current = Current
- ▶ Skinny pipes reduce the flow of water *and* the pressure downstream of the skinny pipe.
Resistor = Skinny Pipe
- ▶ Pumps increase water pressure (and thus flow, through a pipe of given size).
(Voltage) Amplifier = Pump

Electricity as Water

The other slide: the strange bits

- ▶ A pipe with a rubber wall in the middle blocks the flow of water, but lets small variations in water pressure through:
Capacitor = Rubber wall in pipe section
- ▶ There's no good water analogy for a speaker. A surface that moves back and forth in response to changing water pressure? Speakers have cones that move back and forth in response to changes in voltage.
- ▶ One-way valves let water flow through one way, but not the other.
Diode = one-way valve

Outline

Intro

Electronics Background

Oscillation

Oscillation...

... brought to you by Hysteresis

- ▶ Hysteresis is the property of devices that turn on at one point, but off at a different point
- ▶ Thermostats have hysteresis:
Set for 65 degrees, turn on at 63 degrees, turn off at 67 degrees
- ▶ What if it didn't have hysteresis?
- ▶ (Your heater/thermostat system is a very low frequency oscillator!)
- ▶ Like thermostat, many digital circuits use hysteresis
- ▶ "On" is a voltage above $5 * 2/3$ volts.
"Off" is a voltage below $5 * 1/3$ volts.
- ▶ In between? Stays in whichever state it was in last.

Oscillation

Hysteresis *and* Feedback

- ▶ Thermostat controls heater. Heater heats air. Air temperature controls thermostat. Thermostat controls heater...
- ▶ Negative feedback: heating the air turns off the heater, vice versa
- ▶ This negative feedback plus hysteresis keeps the temperature bouncing up and down between the two temperature set points
- ▶ We're going to do the same with electricity.
- ▶ Inverting amplifier with hysteresis (inverting is the negative feedback part)

Oscillator Chip

74HC14: Hex Inverter with Schmitt Trigger

- ▶ Hex = 6
- ▶ Inverter = Inverting amplifier. Given 5v input, sends 0v out.
- ▶ Amplifier is like a pump. This one's a pressure-controlled pump.
- ▶ Schmitt Trigger is the *hysteresis*.
- ▶ Input $> 5v * 2/3$: input is read as high, so output goes low (0v)
- ▶ Input $< 5v * 1/3$: input is read as low, so output goes high (5v)
- ▶ In-between: doesn't change state

Oscillator

The plan

- ▶ Use one inverter from the HC14
- ▶ Feed its output back into its input
- ▶ Hysteresis will make sure that it stays between $5 * 2/3$ and $5 * 1/3$ volts
- ▶ Need to slow it down: skinny pipe and some way to store up the water for a while

The Circuit

How it works

- ▶ Imagine input starts low, output high
- ▶ Current flows through resistor, pushes on capacitor
- ▶ As capacitor gets more and more displaced, it pushes back more and more
- ▶ Eventually the pressure/voltage gets enough to trip the input high
- ▶ Then the output goes low
- ▶ Then current flows through the resistor in the opposite direction
- ▶ This relieves pressure on the capacitor
- ▶ Until...

Buffering

So can we just hook it up?

- ▶ Not yet!
- ▶ If we put the speaker in the circuit, all of our current would just flow out the speaker
- ▶ Use an intermediate stage: a buffer
- ▶ Used LM386 amplifier as buffer
- ▶ (Note: This is not ideal. In the future, I'll just use a stage from the 74HC14 or maybe a 74HC04.)
- ▶ Then to the speaker?

Output Capacitor

Now to the speaker

- ▶ Want to limit the current flowing through the speaker
- ▶ But want changes in pressure to pass through (to make sound)
- ▶ The job for a big capacitor
- ▶ Remember: stretchy rubber membrane in a pipe

Draw Pinout and Circuit on the Board

- ▶ Play!

The End

The End

[◀ Outline](#)